

CAPACITANCE

1. CAPACITANCE

1.1 Concept of Capacitance

Capacitance of a conductor is a measure of its ability to store charge. When a conductor is charged, its potential changes. The increase in potential is directly proportional to the charge given to the conductor.

$$Q \propto V \Rightarrow Q = CV$$

The constant C is known as the capacity or capacitance of the conductor.

Capacitance is a scalar quantity with dimensions $C = \frac{Q}{V} = \frac{Q^2}{W} = \frac{A^2 T^2}{M^1 L^2 T^{-2}} = M^{-1} L^{-2} T^4 A^2$

Unit :- farad, coulomb/volt

The capacitance of a conductor is independent of the charge given or rise in its potential. It is also independent of the nature of material and thickness of the conductor. Theoretically, infinite amount of charge can be given to a conductor.


However, practically the electric field becomes so intense that it causes ionisation of the medium surrounding it. Consequently, the charge on the conductor leaks, reducing its potential.

It is clear that every conductor has a capacity to store charge which is numerically equal to the ratio of charge given to it to the rise in potential, it depends on its shape, size and surrounding medium. However, the capacity of a conductor is small and limited.

It has been found that if a conductor is placed near a charged conductor, then the potential of the charged conductor (relative to the other) decreases and hence it can store more charge, i.e., vicinity of another conductor increases the capacity of a charged conductor.

In case of two conductors (close to each other), if the conductors (called plates) carry equal and opposite charges, the system is called a capacitor or condenser [Figure]. The capacity or capacitance of a capacitor

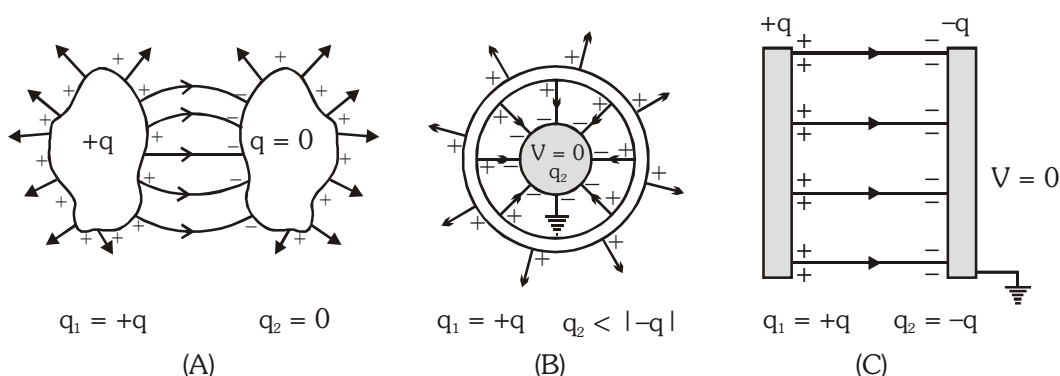is defined as $C = \frac{\text{Magnitude of charge on either plate}}{\text{PD between the plates}}$



The capacity of a capacitor is found to depend on the geometry, i.e., shape and size of the conductors also on, their relative separation and the intervening medium (called dielectric) between them.

Note : Here also on, it must be noted that the charges on the plates of a capacitor are equal and opposite, hence total charge on it is zero and all the electric lines of force which originate from one plate terminate on the other plate. If the charges on the two plates are not equal and opposite, system will still have a capacity but will not be called as a capacitor [e.g. figure (A) and (B)].



1.2 Condenser/Capacitor

A pair of conductors having opposite charges of equal magnitude is defined as condenser.


1.3 Principle of a Condenser

It is based on the fact that capacitance can be increased by reducing the potential keeping the charge constant. Consider a conducting plate M which is given a charge Q such that its potential rises to V then

$$C = \frac{Q}{V}$$


Let us place another identical conducting plate N parallel to it such that charge is induced on plate N (as shown in figure). If V_- is the potential at M due to induced negative charge on N and V_+ is the potential at M due to induced positive charge on N, then
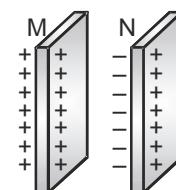
$$C' = \frac{Q}{V'} = \frac{Q}{V + V_+ - V_-}$$



Since $V' < V$ (as the induced negative charge lies closer to the plate M in comparison to induced positive charge). $\Rightarrow C' > C$ Further, if N is earthed from the outer side (see figure) then $V'' = V_+ - V_-$ (\because the entire positive charge flows to the earth)
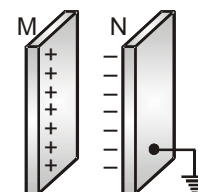
$$C'' = \frac{Q}{V''} = \frac{Q}{V - V_-} \Rightarrow C'' \gg C$$



If an identical earthed conductor is placed in the vicinity of a charged conductor then the capacitance of the charged conductor increases appreciably. This is the principle of a parallel plate capacitor.

2. ENERGY STORED IN A CHARGED CAPACITOR

Let C be the capacitance of a capacitor. On being connected to a battery, it charges to a potential V from zero potential. If q is charge on the capacitor at that time then $q = CV$. Let the battery supply a small amount of charge dq to the capacitor at constant potential V . Then the corresponding small amount of energy stored in capacitor is given by -

$$dU = Vdq = \frac{q}{C} dq \Rightarrow U = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \left[\frac{q^2}{2} \right]_0^Q \Rightarrow U = \frac{Q^2}{2C}$$

where Q is the final charge acquired by the conductor.

$$\text{So, } U = \frac{Q^2}{2C} = \frac{1}{2} \frac{(CV)^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{Q}{V} \right) V^2 = \frac{1}{2} QV$$

$$\therefore \boxed{U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV}$$

Note :- Work done by battery = Charge supplied \times potential

$$\boxed{W_{\text{Battery}} = QV = CV^2 = \frac{Q^2}{C}}$$



3. THE CAPACITANCE OF A SPHERICAL CONDUCTOR / CAPACITOR

3.1 Isolated Sphere

When a charge Q is given to an isolated spherical conductor, its potential rises.

$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{R}$$


$$\text{or, } C = \frac{Q}{V} = 4\pi\epsilon_0 R$$

If the conductor is placed in a certain medium then,

$$C_{\text{medium}} = 4\pi\epsilon R \quad \text{or} \quad C_{\text{medium}} = 4\pi\epsilon_0 \epsilon_r R$$

Capacitance depends upon :

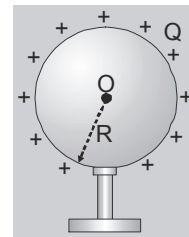- size and Shape of Conductor
- surrounding medium
- presence of other conductors nearby.



3.2 Outer sphere is earthed (Spherical Capacitor)

When a charge Q is given to the inner sphere it is uniformly distributed on its surface. A charge $-Q$ is induced on the inner surface of outer sphere. The charge $+Q$ induced on the outer surface of outer sphere flows to earth as it is grounded.

$$E = 0 \text{ for } r < R_1 \quad \text{and} \quad E = 0 \text{ for } r > R_2$$

$$\text{Potential of inner sphere } V_1 = \frac{Q}{4\pi\epsilon_0 R_1} + \frac{-Q}{4\pi\epsilon_0 R_2} \Rightarrow \frac{Q}{4\pi\epsilon_0} \left(\frac{R_2 - R_1}{R_1 R_2} \right)$$


As outer surface is earthed so potential $V_2 = 0$

$$\text{Potential difference between the plates } V = V_1 - V_2 = \frac{Q}{4\pi\epsilon_0} \frac{(R_2 - R_1)}{R_1 R_2}$$

$$\text{So } C = \frac{Q}{V} = 4\pi\epsilon_0 \frac{R_1 R_2}{R_2 - R_1} \quad (\text{in air or vacuum})$$

In presence of medium between plate
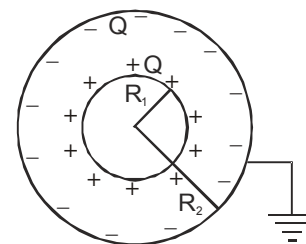
$$C = 4\pi\epsilon_r \epsilon_0 \frac{R_1 R_2}{R_2 - R_1}$$





3.3 Inner sphere is earthed

Here, the system is equivalent to a spherical capacitor of inner and outer radii R_1 and R_2 respectively and a spherical conductor of radius R_2 in parallel. This is because charge Q given to outer sphere gets distributed in such a way that for the outer sphere :

$$\text{Charge on the inner side } q_{\text{in}} = \frac{R_1}{R_2} Q \quad \text{and}$$
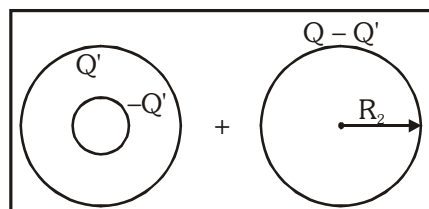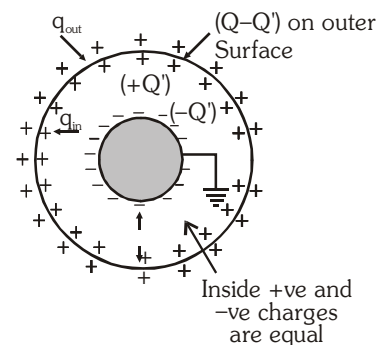
$$\text{Charge on the outer side } q_{\text{out}} = Q - \frac{R_1}{R_2} Q = \frac{(R_2 - R_1)}{R_2} Q$$



$$\text{So total capacity of the system is } C = 4\pi\epsilon_0 \frac{R_1 R_2}{(R_2 - R_1)} + 4\pi\epsilon_0 R_2 = \frac{4\pi\epsilon_0 R_2^2}{(R_2 - R_1)}$$

$$C = \frac{4\pi\epsilon_0 R_2^2}{(R_2 - R_1)}$$



GOLDEN KEY POINTS

- Work done by a battery $W_b = (\text{charge delivered by battery}) \times (\text{emf}) = QV$ but


$$\text{Energy stored in conductor} = \frac{1}{2} QV$$

so 50% of the energy supplied by the battery is lost in the form of heat.





- The amount of energy stored depends on the size of the conductor.
- When a capacitor C charged upto a voltage V is discharged by means of any resistance

$$\text{then heat loss} = \frac{CV^2}{2} \text{ (independent of } R\text{)}$$

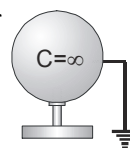- As the potential of the Earth is assumed to be zero, practically, capacity of earth or a conductor connected to earth will be infinite $C = \frac{q}{V} = \frac{q}{0} = \infty$



- Theoretically, capacity of the Earth $C = 4\pi\epsilon_0 R = \frac{1}{9 \times 10^9} \times 64 \times 10^5 = 711 \mu\text{F}$

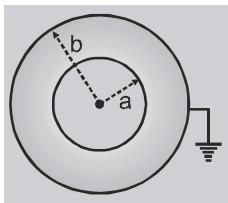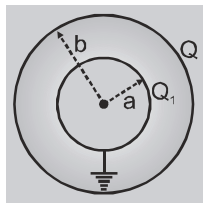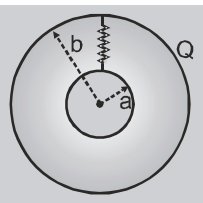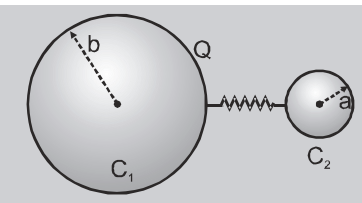Spherical capacitor outer plate is earthed	Inner plate is earthed and outer plate is given a charge	Connected and outer plate is given a charge	Connected spheres
			
$C = \frac{4\pi\epsilon_0 ab}{b-a}$ ($b > a$)	$C = \frac{4\pi\epsilon_0 b^2}{b-a}$ ($b > a$)	$C = 4\pi\epsilon_0 b$	$C = C_1 + C_2$ $C = 4\pi\epsilon_0(a+b)$

Illustrations

Illustration 1.

A capacitor gets a charge of $50 \mu\text{C}$ when it is connected to a battery of emf 5 V . Calculate the capacity of the capacitor.

Solution

$$\text{Capacity of the capacitor } C = \frac{Q}{V} = \frac{50 \times 10^{-6}}{5} = 10 \mu\text{F}$$

Illustration 2.

The plates of a capacitor are charged to a potential difference of 100 V and then connected across a resistor. The potential difference across the capacitor decays exponentially with respect to time. After one second, the potential difference between the plates of the capacitor is 80 V . What is the fraction of the stored energy which has been dissipated ?

Solution

$$\text{Energy losses } \Delta U = \frac{1}{2} CV_0^2 - \frac{1}{2} CV^2$$

$$\text{Fractional energy loss } \frac{\Delta U}{U_0} = \frac{\frac{1}{2} CV_0^2 - \frac{1}{2} CV^2}{\frac{1}{2} CV_0^2} = \frac{V_0^2 - V^2}{V_0^2} = \frac{(100)^2 - (80)^2}{(100)^2} = \frac{20 \times 180}{(100)^2} = \frac{9}{25}$$



Illustration 3.

Two uniformly charged spherical drops each at a potential V coalesce to form a larger drop. If the capacity of each smaller drop is C then find the capacity and potential of larger drop.

Solution

When drops coalesce to form a larger drop then total charge and volume remains conserved. If r is the radius and q is the charge on smaller drop then $C = 4\pi\epsilon_0 r$ and $q = CV$

$$\text{Equating volume we get} \quad \frac{4}{3}\pi R^3 = 2 \times \frac{4}{3}\pi r^3 \Rightarrow R = 2^{1/3}r$$

$$\text{Capacitance of larger drop} \quad C' = 4\pi\epsilon_0 R = 2^{1/3}C$$

$$\text{Charge on larger drop} \quad Q = 2q = 2CV$$

$$\text{Potential of larger drop} \quad V' = \frac{Q}{C'} = \frac{2CV}{2^{1/3}C} = 2^{2/3}V.$$

Illustration 4.

The stratosphere acts as a conducting layer for the earth. If the stratosphere extends beyond 50 km from the surface of earth, then calculate the capacitance of the spherical capacitor formed between the stratosphere and earth's surface. Take radius of earth as 6400 km.

Solution

$$\text{The capacitance of a spherical capacitor is } C = 4\pi\epsilon_0 \left(\frac{ab}{b-a} \right)$$

$$b = \text{radius of the stratosphere layer} = 6400 \text{ km} + 50 \text{ km} = 6450 \text{ km} = 6.45 \times 10^6 \text{ m}$$

$$a = \text{radius of earth} = 6400 \text{ km} = 6.4 \times 10^6 \text{ m}$$

$$\therefore C = \frac{1}{9 \times 10^9} \times \frac{6.45 \times 10^6 \times 6.4 \times 10^6}{(6.45 \times 10^6 - 6.4 \times 10^6)} = 0.092 \text{ F}$$

Illustration 5.

Calculate the energy of a sphere of radius 2 cm if it is charged to 300 volts.

Solution

$$\text{Stored energy } U = \frac{1}{2}CV^2 = \frac{1}{2}(4\pi\epsilon_0 R)V^2 = \frac{RV^2}{2k} = \frac{2 \times 10^{-2} \times 300 \times 300}{2 \times 9 \times 10^9} = 10^{-7} \text{ J.}$$

Illustration 6.

Two insulated conductors are charged by transferring electrons from one conductor to another. A potential difference of 100 V is produced by transferring 6.25×10^{15} electrons from one conductor to the other. The capacity of the system will be.

Solution

$$Q = CV \Rightarrow C = \frac{Q}{V} = \frac{ne}{V}$$


$$\text{Given } V = 100 \text{ volts ; } n = 6.25 \times 10^{15}$$

$$\therefore C = \frac{6.25 \times 10^{15} \times 1.6 \times 10^{-19}}{100} = 10 \mu\text{F}$$



BEGINNER'S BOX-1

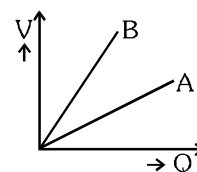
1. A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the capacitor is
2. A capacitor of capacitance C has a charge Q . The net charge on a capacitor is alwaysIt stores..... energy.
3. A capacitor of capacity C has charge Q and stored energy is W . If the charge is increased to $2Q$ then what will be the stored energy ?
4. Eight drops of mercury of equal radii and possessing equal charges combine to form a big drop. Then the capacitance of the bigger drop compared to each individual drop is
5. The capacitance of a spherical condenser whose inner sphere is grounded is $1\mu\text{F}$. If the spacing between the two spheres is 1 mm then what is the radius of the outer sphere ?
6. When 2×10^{16} electrons are transferred from one conductor to another, a potential difference of 10 V appears between the conductors. Calculate the capacitance of the two conductors system.
7. The graph shows the variation of voltage V across the plates of two capacitors A & B with charge Q .
Which of the two capacitors has larger capacitance ?
8. For flash pictures, a photographer uses a $30\mu\text{F}$ capacitor and a charger that supplies $3 \times 10^3\text{ volt}$. Calculate the charge and the energy spent for each flash.
9. Two capacitors C_1 and C_2 have equal amount of energy stored in them. What is the ratio of potential differences across their plates ?



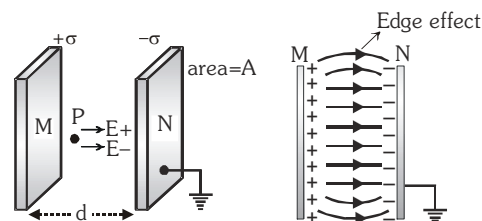4. PARALLEL PLATE CAPACITOR

• Capacitance

It consists of two metallic plates M and N each of area A at a separation d . Plate M is positively charged and plate N is earthed. If ϵ_r is the dielectric constant of the material medium and E is the field at a point P that exists between the two plates, then



Step - I : Finding electric field $E = E_+ + E_- = \frac{\sigma}{2\epsilon} + \frac{\sigma}{2\epsilon} = \frac{\sigma}{\epsilon} = \frac{\sigma}{\epsilon_0\epsilon_r}$ [$\epsilon = \epsilon_0\epsilon_r$]

Step - II : Finding potential difference $V = Ed = \frac{\sigma}{\epsilon_0\epsilon_r} d = \frac{qd}{A\epsilon_0\epsilon_r}$ ($\because E = \frac{V}{d}$ and $\sigma = \frac{q}{A}$)

Step - III : Finding capacitance $C = \frac{q}{V} = \frac{\epsilon_r\epsilon_0A}{d}$

If the medium between the plates is air or vacuum, then $\epsilon_r = 1 \Rightarrow C_0 = \frac{\epsilon_0A}{d}$
so $C = \epsilon_r C_0 = KC_0$. (where $\epsilon_r = K$ = dielectric constant)

• Force between the plates

The two plates of a capacitor attract each other because they are oppositely charged.

Electric field due to positive plate $E_1 = \frac{\sigma}{2\epsilon_0} = \frac{Q}{2\epsilon_0A}$

Force on negative charge $-Q$ is $F = -Q E_1 = -\frac{Q^2}{2\epsilon_0A}$

Magnitude of force $F = \frac{Q^2}{2\epsilon_0A} = \frac{1}{2}\epsilon_0AE^2$ E = Net electric field between the plates of capacitor.

Force per unit area or energy density or electrostatic pressure = $\frac{F}{A} = u = P = \frac{1}{2}\epsilon_0 E^2$



5. EFFECT OF DIELECTRIC

- The insulators in which microscopic local displacement of charges take place in the presence of electric field are known as dielectrics.
- Dielectrics are non conductors upto a certain value of field depending on its nature. If the field exceeds this limiting value called dielectric strength, they lose their insulating property and begin to conduct.
- Dielectric strength is defined as the maximum value of electric field that a dielectric can withstand without breakdown. Unit is volt/metre. Dimensions : $[M^1 L^1 T^{-3} A^{-1}]$

Polar dielectrics

- In the absence of external field the centres of positive and negative charges do not coincide in these atoms or molecules due to asymmetric shapes of molecules.
- Each molecule has a permanent dipole moment.
- The dipoles are randomly oriented ; so average dipole moment per unit volume of polar dielectric in the absence of external field is zero.
- In the presence of external field dipoles tend to align in the direction of field.

Ex. Water, Alcohol, HCl, NH_3 etc.

Non-polar dielectrics

- In the absence of external field the centres of positive and negative charges coincide in these atoms or molecules because they are symmetric.
- The dipole moment is zero in normal state.
- In the presence of external field they acquire induced dipole moment.

Ex. Nitrogen, Oxygen, Benzene, Methane etc.

Polarisation :

The alignment of dipole moments of permanent or induced dipoles in the direction of applied electric field is called polarisation.

- **Polarisation vector (\vec{P})**



It is a vector quantity which describes the extent to which molecules of dielectric of become polarized by an electric field or oriented in the direction of field.

$$\vec{P} = \text{the dipole moment per unit volume of dielectric} = n \vec{p}$$


where n is number of atoms per unit volume of dielectric and \vec{p} is dipole moment of an atom or molecule.

$$\vec{P} = n \vec{p} = \frac{q_i d}{A d} = \left(\frac{q_i}{A} \right) = \sigma_i = \text{induced surface charge density.}$$
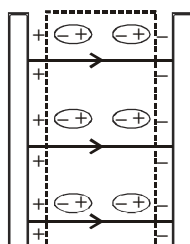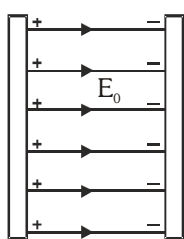
$$\text{Unit of } \vec{P} \text{ is } C/m^2 \quad \text{Dimension : } [L^{-2} T^1 A^1]$$



Dielectric slab

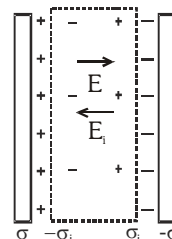

Let E_0 , V_0 , C_0 be the electric field, potential difference and capacitance in the absence of dielectric. Let E , V , C be the corresponding quantities in the presence of the dielectric respectively.

Electric field in the absence of dielectric $E_0 = \frac{V_0}{d} = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$

Electric field in the presence of dielectric $E = E_0 - E_i = \frac{\sigma - \sigma_i}{\epsilon_0} = \frac{Q - Q_i}{A\epsilon_0} = \frac{V}{d}$

Capacitance in the absence of dielectric $C_0 = \frac{Q}{V_0}$

Capacitance in the presence of dielectric $C = \frac{Q - Q_i}{V}$


Dielectric constant or relative permittivity K or $\epsilon_r = \frac{E_0}{E} = \frac{V_0}{V} = \frac{C}{C_0} = \frac{Q}{Q - Q_i} = \frac{\sigma}{\sigma - \sigma_i} = \frac{\epsilon}{\epsilon_0}$

From $K = \frac{Q}{Q - Q_i} \Rightarrow Q_i = Q \left(1 - \frac{1}{K}\right)$ and $K = \frac{\sigma}{\sigma - \sigma_i} \Rightarrow \sigma_i = \sigma \left(1 - \frac{1}{K}\right)$

Note :- Above relation is applicable only for PPC.

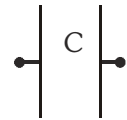6. DIELECTRIC SLAB INSIDE A PARALLEL PLATE CAPACITOR

In case of a parallel plate capacitor $C = \frac{\epsilon_0 A}{d}$



If capacitor is partially filled with dielectric

When the capacitor is filled partially with dielectric between plates, the thickness of dielectric slab is t ($t < d$) :


For an capacitor, the field E_0 is given by $E_0 = \frac{\sigma}{\epsilon_0}$, exists in the space d .

On inserting a slab of thickness t , a field $E = \frac{E_0}{\epsilon_r}$ appears inside the slab and a field E_0 exists in the remaining

space $(d - t)$. If V is the potential difference between the plates then $V = E_0(d - t) + Et$

$\Rightarrow V = E_0 \left[d - t + \left(\frac{E}{E_0} \right) t \right] \because \frac{E_0}{E} = \epsilon_r = \text{Dielectric constant}$

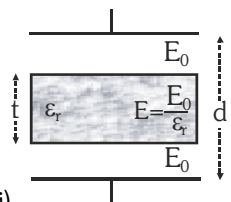
$\Rightarrow V = \frac{\sigma}{\epsilon_0} \left[d - t + \frac{t}{\epsilon_r} \right] = \frac{q}{A\epsilon_0} \left[d - t + \frac{t}{\epsilon_r} \right] \Rightarrow C = \frac{q}{V} = \frac{\epsilon_0 A}{d - t \left(1 - \frac{1}{\epsilon_r} \right)} = \frac{\epsilon_0 A}{d - t \left(1 - \frac{1}{\epsilon_r} \right)} \dots (i)$



If the dielectric medium is present between the entire space.


then $t = d$

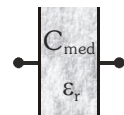Now from equation (i) $C_{\text{medium}} = \frac{\epsilon_0 \epsilon_r A}{d}$



If capacitor is partially filled with a conducting slab of thickness t ($t < d$).

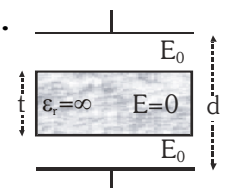$\because \epsilon_r = \infty$ for conductor, so $C = \frac{\epsilon_0 A}{d - t \left(1 - \frac{1}{\infty} \right)} = \frac{\epsilon_0 A}{(d - t)}$



7. ELECTROSTATIC PRESSURE

Force due to electrostatic pressure is directed outwards normal to the surface .

Force on a small element ds of a charged conductor

$$dF = (\text{Charge on } ds) \times \text{Electric field} = (\sigma ds) \frac{\sigma}{2\epsilon_0} = \frac{\sigma^2}{2\epsilon_0} ds$$


Inside $E_1 - E_2 = 0 \Rightarrow E_1 = E_2$

$$\text{Just outside } E = E_1 + E_2 = 2E_2 \Rightarrow E_2 = \frac{\sigma}{2\epsilon_0}$$

(E_1 is field due to charge on the element ds of the surface and E_2 is field due to rest of the sphere).

The electric force acting per unit area of charged surface is defined as electrostatic pressure.
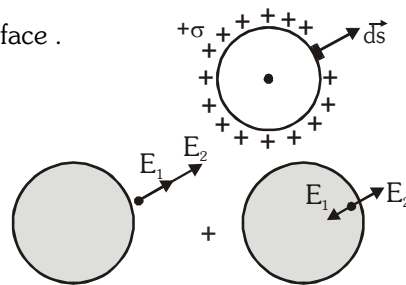
$$P_{\text{electrostatic}} = \frac{dF}{dS} = \frac{\sigma^2}{2\epsilon_0}$$



7.1 Equilibrium of charged liquid surfaces (Soap bubble)


Pressures (forces) act on a charged soap bubble , due to

- (i) Surface tension P_T (inward)
- (ii) Air outside the bubble P_o (inward)
- (iii) Electrostatic pressure P_e (outward)
- (iv) Air inside the bubble P_i (outward)

In the state of equilibrium, inward pressure = outward pressure $P_T + P_o = P_i + P_e$

Excess pressure of air inside the bubble (P_{ex}) = $P_i - P_o = P_T - P_e$
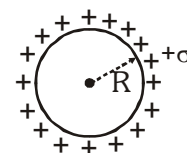
$$\text{but } P_T = \frac{4T}{r} \text{ and } P_e = \frac{\sigma^2}{2\epsilon_0} \Rightarrow P_{ex} = \frac{4T}{r} - \frac{\sigma^2}{2\epsilon_0} \text{ if } P_i = P_o \text{ then } \frac{4T}{r} = \frac{\sigma^2}{2\epsilon_0}$$



7.2 Combination of Identical Charged Tiny Drops


Let , number of tiny drops = N

for each **tiny** drop

(r, q, C, σ, E, V)

for **Big** drop

($R, Q, C_B, \sigma_B, E_B, V_B$)

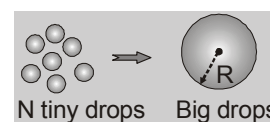

(i) Charge conservation $Q = Nq$

(ii) Volume conservation $\frac{4}{3}\pi N.r^3 = \frac{4}{3}\pi R^3$

Hence $R = N^{1/3} r$, $Q = Nq$ $\therefore C_B = N^{1/3} C$, $\sigma_B = N^{1/3} \sigma$, $E_B = N^{1/3} E$, $V_B = N^{2/3} V$

- When a soap bubble is charged (either positive or negative) then the size (radius) increases some what and

Positive charge \Rightarrow mass \downarrow ; Negative charge \Rightarrow mass \uparrow

7.3 Energy Density (u)

Energy associated per unit volume of electric field is defined as energy density.

$$u = \frac{dW}{dV} = \frac{\epsilon_0 E^2}{2} = \frac{\sigma^2}{2\epsilon_0} \text{ J/m}^3$$

$$U = \int u.dV = \frac{\epsilon_0}{2} \int E^2 dV ; V \text{ is the volume of electric field.}$$




GOLDEN KEY POINTS


- If one of the plates of a parallel plate capacitor slides parallel to the other then C decreases (As overlapping area decreases).

$$C = \frac{\epsilon_0 A}{d}, \text{ where}$$

A = overlapping area

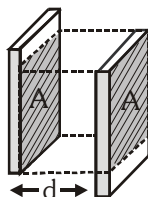

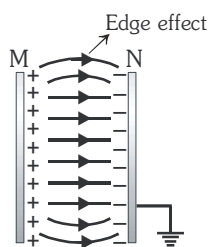- If both the plates of a parallel plate capacitor are touched with each other then the resultant charge and potential difference becomes zero.
- Electric field between the plates of a capacitor is shown in figure. Non-uniformity of electric field at the boundaries of the plates is negligible if the distance between the plates is very small as compared to the length of the plates.



\vec{E} = uniform between the plates

\vec{E} = non-uniform at the edges

- Capacitance of a parallel plate capacitor does not depend on thickness and nature of metal of plates.
- For a parallel plate capacitor :
 - Intensity of electric field between the plates $E = \frac{\sigma}{\epsilon_0} = \frac{V}{d}$ (uniform)
 - Force between the plates $= \frac{CV^2}{2d} = \frac{QE}{2}$ ($E \rightarrow$ Electric field)
 - Pressure on the plates $= \frac{\sigma^2}{2\epsilon_0}$
- If nothing is mentioned then assume the battery to be disconnected and Q is constant.
- A parallel plate capacitor is connected to a battery ($V = \text{const.}$) and a slab of dielectric constant ϵ_r is inserted between the plates then the total energy delivered by the battery is divided into two parts :
 - Half is used to insert the slab (work is done by field)
 - Half is stored in the form of electrostatic potential energy.

Battery disconnected (Q is constant)

Change executed	Q	$V = \frac{Q}{C}$ $V \propto \frac{1}{C}$	$E = \frac{Q}{\epsilon_0 \epsilon_r A}$	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$U = \frac{Q^2}{2C}$ $U \propto \frac{1}{C}$
Filled with medium	Unchanged	Decreases	Decreases	Increases	Decreases
Distance is Decreased	Unchanged	Decreases	Unchanged	Increases	Decreases
Area is Increased	Unchanged	Decreases	Decreases	Increases	Decreases



Battery still connected (V is constant)

Change executed	$Q = CV$ $Q \propto C$	V constant	$E = \frac{V}{d}$ $E \propto \frac{1}{d}$	$C = \frac{\epsilon_0 \epsilon_r A}{d}$	$U = \frac{1}{2} CV^2$ $U \propto C$
Filled with medium	Increases	Unchanged	Unchanged	Increases	Increases
Distance is Decreased	Increases	Unchanged	Increases	Increases	Increases
Area is Increased	Increases	Unchanged	Unchanged	Increases	Increases

- If a small charge q is moved along a closed path in the field between the plates of a parallel-plate capacitor, no work will be done by the agent.
- Two positively charged identical plates placed parallel to each other form a parallel plate capacitor.
- If a capacitor is connected across a battery, then the charges will be equal in magnitude even if the plates are of different sizes.

Illustrations

Illustration 7.

If the distance between the plates of a capacitor of capacitance C_1 is halved and the area of plates is doubled then what will be the capacitance ?

Solution

$$C = \frac{\epsilon_0 A}{d} \Rightarrow \frac{C_1}{C_2} = \frac{A_1}{A_2} \frac{d_2}{d_1} = \frac{A_1}{2A_1} \times \left(\frac{1}{d_1} \right) \left(\frac{d_1}{2} \right) = \frac{1}{4} \Rightarrow C_2 = 4C_1$$

Illustration 8.

A capacitor has two circular plates whose radii are 8 cm each and distance between them is 1mm. When mica slab (dielectric constant = 6) is placed between the plates, calculate the capacitance and the energy stored when it is given a potential of 150 volts.

Solution

$$\text{Area of each plate} = \pi r^2 = \pi \times (8 \times 10^{-2})^2 = 0.0201 \text{ m}^2 \quad \text{and} \quad d = 1 \text{ mm} = 1 \times 10^{-3} \text{ m}$$

$$\text{Capacity of capacitor} \quad C = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{8.85 \times 10^{-12} \times 6 \times 0.0201}{1 \times 10^{-3}} = 1.068 \times 10^{-9} \text{ F}$$

$$\text{Potential difference} \quad V = 150 \text{ volt}$$

$$\text{Energy stored} \quad U = \frac{1}{2} CV^2 = \frac{1}{2} \times (1.068 \times 10^{-9}) \times (150)^2 = 1.2 \times 10^{-5} \text{ J}$$

Illustration 9.

A parallel-plate capacitor is formed of two plates, each of area 100 cm^2 , separated by a distance of 1mm. A dielectric of dielectric constant 5.0 and dielectric strength $1.9 \times 10^7 \text{ V/m}$ is introduced between the plates. Find the maximum charge that can be stored in the capacitor without causing any dielectric breakdown.

Solution

If the charge on the capacitor = Q

$$\text{the surface charge density } \sigma = \frac{Q}{A} \quad \text{and the electric field} = \frac{Q}{KA\epsilon_0}.$$

This electric field should not exceed the dielectric strength $1.9 \times 10^7 \text{ V/m}$.

$$\therefore \text{ if the maximum charge which can be given is } Q \text{ then } \frac{Q}{KA\epsilon_0} = 1.9 \times 10^7 \text{ V/m}$$

$$\therefore A = 100 \text{ cm}^2 = 10^{-2} \text{ m}^2 \Rightarrow Q = (5.0) \times (10^{-2}) \times (8.85 \times 10^{-12}) \times (1.9 \times 10^7) = 8.4 \times 10^{-6} \text{ C}.$$



Illustration 10.

The distance between the plates of a parallel-plate capacitor is 0.05 m. A field of 3×10^4 V/m is established between the plates. It is disconnected from the battery and an uncharged metal plate of thickness 0.01 m is inserted into the gap between the plates. Find the potential difference of the capacitor (i) before the introduction of the metal plate and (ii) after its introduction. What would be the potential difference if a plate of dielectric constant $K = 2$ is introduced in place of metal plate ?

Solution

(i) In case of a capacitor as $E = (V/d)$, the potential difference between the plates before the introduction of metal plate

$$V = E \times d = 3 \times 10^4 \times 0.05 = 1.5 \text{ kV}$$

(ii) Now as battery is removed after charging, capacitor is isolated so $q = \text{constant}$. If C' and V' are the capacity

and potential after the introduction of plate then, $q = CV = C'V'$ i.e., $V' = \frac{C}{C'}V$

$$\text{And as } C = \frac{\epsilon_0 A}{d} \text{ and } C' = \frac{\epsilon_0 A}{(d-t) + (t/K)}, \quad V' = \frac{(d-t) + (t/K)}{d} V$$

$$\text{So in case of metal plate as } K = \infty, \quad V_M = \left[\frac{d-t}{d} \right] V = \left[\frac{0.05-0.01}{0.05} \right] 1.5 = 1.2 \text{ kV}$$

And if instead of metal plate a dielectric with $K = 2$ is

$$\text{introduced then } V_D = \left[\frac{(0.05-0.01) + (0.01/2)}{0.05} \right] \times 1.5 = 1.35 \text{ kV}.$$

Illustration 11.

A parallel plate capacitor has a potential 20 kV and capacitance 2×10^{-4} μF . If area of each plate is 0.01 m^2 and distance between them is 2 mm then find the -

- (a) potential gradient (b) dielectric constant of medium (c) energy

Solution

$$(a) \quad \text{potential gradient} = \frac{V}{d} = \frac{20000}{0.002} = 1 \times 10^7 \text{ V/m}$$

$$(b) \quad C = \frac{\epsilon_0 \epsilon_r A}{d} \Rightarrow \epsilon_r = \frac{Cd}{\epsilon_0 A} = \frac{2 \times 10^{-10} \times 2 \times 10^{-3}}{8.85 \times 10^{-12} \times 0.01} = 4.52$$

$$(c) \quad U = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times 10^{-10} \times (20000)^2 = 4 \times 10^{-2} \text{ J}$$

Illustration 12.

Twenty seven charged water droplets, each of radius 10^{-3} m and having a charge of 10^{-12} C, coalesce to form a single drop. Calculate the potential of the bigger drop.

Solution

$$\text{Volume of bigger drop} = N \times \text{volume of smaller drop} \Rightarrow \frac{4}{3} \pi R^3 = N \times \frac{4}{3} \pi r^3 \Rightarrow R^3 = Nr^3 \Rightarrow R = N^{1/3} r$$


$$R = (27)^{1/3} r = 3r$$

$$\text{Potential of bigger drop } V = \frac{kQ}{R} = \frac{kNq}{3r} = \frac{9 \times 10^9 \times 27 \times 10^{-12}}{3 \times 10^{-3}} = 81 \text{ volts}$$



BEGINNER'S BOX-2

- The plate separation in a parallel plate capacitor is d and plate area is A . If it is charged to V volts then calculate the work done in increasing the plate separation to $2d$.
- Three parallel metallic plates, each of area A are kept as shown in the figure and charges Q_1 , Q_2 and Q_3 are given to them. Edge effects are negligible. Calculate the charges on the two outermost surfaces 'a' and 'f'.

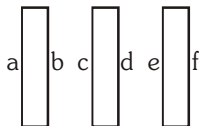

- (A) $\frac{Q_1 + Q_2 + Q_3}{2}$ (B) $\frac{Q_1 + Q_2 + Q_3}{3}$ (C) $\frac{Q_1 - Q_2 + Q_3}{3}$ (D) $\frac{Q_1 - Q_2 + Q_3}{2}$
- A capacitor has a capacitance of 50 pF , which increases to 175 pF with a dielectric material between its plates. What is the dielectric constant of the material ?
 - A parallel plate capacitor has rectangular plates with dimensions $6.0 \text{ cm} \times 8.0 \text{ cm}$. If the plates are separated by a sheet of teflon ($K = 2.1$) 1.5 mm thick, how much energy is stored in the capacitor when it is connected to a 12 V battery ?
 - The distance between the plates of a parallel plate capacitor is ' d '. Another thick metal plate of thickness $d/2$ and area same as that of plates is so placed between the plates, that it does not touch them. The capacity of the resulting capacitor :-
(A) remains the same (B) becomes double (C) becomes half (D) becomes one fourth
 - The capacity and the energy stored in a parallel plate condenser with air between its plates are respectively C_0 and W_0 . If the air between the plates is replaced by glass (dielectric constant = 5) find the capacitance of the condenser and the energy stored in it.
 - A parallel plate capacitor is to be designed with a voltage rating 1 kV using a material of dielectric constant 10 and dielectric strength 10^6 Vm^{-1} . What minimum area of the plates is required to have a capacitance of 88.5 pF ?
 - A capacitor of capacitance $10 \text{ }\mu\text{F}$ is connected to battery of emf 20 V . Without disconnecting the source a dielectric ($K=4$) is introduced to fill the space between the two plates of the capacitor. Calculate the –
(a) charge before the dielectric was introduced.
(b) charge after the dielectric is introduced.
 - An air capacitor of capacity $C = 10 \text{ }\mu\text{F}$ is connected to a constant voltage battery of 10 V . Now the space between the plates is filled with a liquid of dielectric constant 5 . Calculate additional charge which flows from the battery to the capacitor.
 - If the distance between the plates of a capacitor is d and potential difference is V then what is the energy density between the plates ?
 - 64 droplets of mercury each of radius r and carrying charge q , coalesce to form a big drop. Compare the surface density of charge of each drop with that of the big drop.

8. COMBINATION OF CAPACITORS


• Capacitors in series:

In this arrangement of capacitors, charge has no alternative path(s) to flow.

- The charge on each capacitor is equal
i.e. $Q = C_1 V_1 = C_2 V_2 = C_3 V_3$
- The total potential difference across AB is shared by the capacitors in the inverse ratio of their respective capacitances $V = V_1 + V_2 + V_3$

If C_s is the net capacitance of the series combination, then
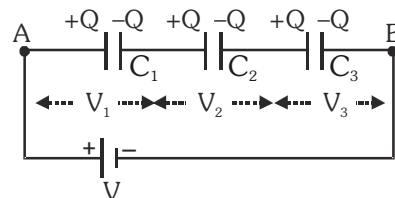
$$\frac{Q}{C_s} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \Rightarrow \boxed{\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$



- **Capacitors in parallel**

In such an arrangement of capacitors, charge has an alternative path(s) to flow.


- (i) The potential difference across each capacitor is same and equal to the

total potential difference applied. i.e. $V=V_1=V_2=V_3 \Rightarrow V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_3}{C_3}$

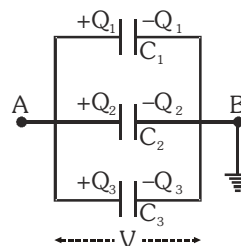- (ii) The total charge Q is shared by the capacitor in the direct ratio of their respective capacitances. $Q = Q_1 + Q_2 + Q_3$

If C_p is the net capacitance for the parallel combination of capacitors, then :

$$C_p V = C_1 V + C_2 V + C_3 V \Rightarrow \boxed{C_p = C_1 + C_2 + C_3}$$



- **Combination of Dielectric Slabs**

- **Plate Separation Division**

- (i) Plate Separation gets divided and area remains same.

- (ii) Capacitors are in series.


- (iii) Individual capacitances are $C_1 = \frac{\epsilon_0 \epsilon_{r_1} A}{d_1}$, $C_2 = \frac{\epsilon_0 \epsilon_{r_2} A}{d_2}$

These two are in series

$$\therefore \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C} = \frac{d_1}{\epsilon_0 \epsilon_{r_1} A} + \frac{d_2}{\epsilon_0 \epsilon_{r_2} A} \Rightarrow \frac{1}{C} = \frac{1}{\epsilon_0 A} \left[\frac{d_1 \epsilon_{r_2} + d_2 \epsilon_{r_1}}{\epsilon_{r_1} \epsilon_{r_2}} \right]$$

$$\Rightarrow C = \epsilon_0 A \left[\frac{\epsilon_{r_1} \epsilon_{r_2}}{d_1 \epsilon_{r_2} + d_2 \epsilon_{r_1}} \right]$$

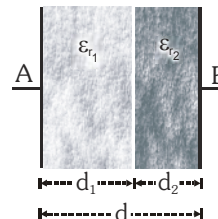Special case : If $d_1 = d_2 = \frac{d}{2} \Rightarrow \boxed{C = \frac{\epsilon_0 A}{d} \left[\frac{2 \epsilon_{r_1} \epsilon_{r_2}}{\epsilon_{r_1} + \epsilon_{r_2}} \right]}$



- **Plate Area Division**


- (i) Plate area gets divided and distance between them remains same.

- (ii) Capacitors are in parallel.

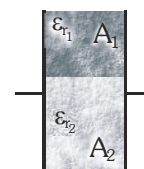- (iii) Individual capacitances are $C_1 = \frac{\epsilon_0 \epsilon_{r_1} A_1}{d}$, $C_2 = \frac{\epsilon_0 \epsilon_{r_2} A_2}{d}$

These two are in parallel so $C = C_1 + C_2 = \frac{\epsilon_0 \epsilon_{r_1} A_1}{d} + \frac{\epsilon_0 \epsilon_{r_2} A_2}{d} = \frac{\epsilon_0}{d} (\epsilon_{r_1} A_1 + \epsilon_{r_2} A_2)$


Special case : If $A_1 = A_2 = \frac{A}{2}$ Then $\boxed{C = \frac{\epsilon_0 A}{d} \left(\frac{\epsilon_{r_1} + \epsilon_{r_2}}{2} \right)}$



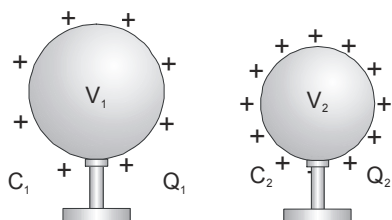
9. SHARING OF CHARGES

When two charged conductors are connected by a conducting wire then charge flows from a conductor at higher potential to that at lower potential. This flow of charge stops when the potential of both conductors become equal.

Let the amounts of charges after the conductors are connected be Q_1' and Q_2' respectively and their common potential be V then



(Before connection)

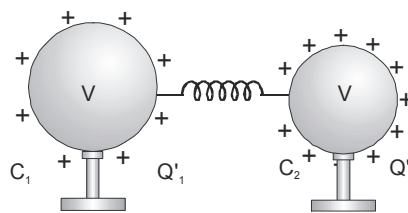

(After connection)



- **Common potential**

According to the law of conservation of charge $Q_{\text{before connection}} = Q_{\text{after connection}}$

$$C_1 V_1 + C_2 V_2 = C_1 V + C_2 V$$

Common potential after connection $V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$

- **Charges after connection**

$$Q_1' = C_1 V = C_1 \left(\frac{Q_1 + Q_2}{C_1 + C_2} \right) = \left(\frac{C_1}{C_1 + C_2} \right) Q \quad (Q = \text{Total charge on the system})$$

$$Q_2' = C_2 V = C_2 \left(\frac{Q_1 + Q_2}{C_1 + C_2} \right) = \left(\frac{C_2}{C_1 + C_2} \right) Q$$

Ratio of the charges after redistribution $\frac{Q_1'}{Q_2'} = \frac{C_1 V}{C_2 V} = \frac{R_1}{R_2}$ (in case of spherical conductors)

- **Loss of energy in charge redistribution**

When charge flows through the conducting wire certain **energy is lost** and electrical energy is converted into heat energy, so change in energy of this system is,

$$\Delta U = U_f - U_i \Rightarrow \left(\frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 \right) - \left(\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) \Rightarrow \Delta U = -\frac{1}{2} \left(\frac{C_1 C_2}{C_1 + C_2} \right) (V_1 - V_2)^2$$

Here negative sign indicates that energy of the system decreases in the process.

GOLDEN KEY POINTS

- If space between the plates is divided equally into two parts


(i) Distance-wise division $C_e = (\text{Harmonic mean of } \epsilon_{r_1} \text{ \& } \epsilon_{r_2}) \times C = \left(\frac{2\epsilon_{r_1} \epsilon_{r_2}}{\epsilon_{r_1} + \epsilon_{r_2}} \right) C$

(ii) Area-wise division $C_e = (\text{Arithmetic mean of } \epsilon_{r_1} \text{ \& } \epsilon_{r_2}) \times C = \left(\frac{\epsilon_{r_1} + \epsilon_{r_2}}{2} \right) C$


Where C = capacity of PPC without any dielectric

- If $V_1 = V_2$ then neither charge flows nor energy is lost when two charged conductors are connected.
- A charged capacitor of energy U is connected to an identical uncharged capacitor.

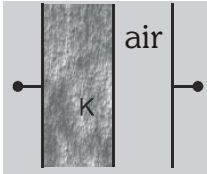
Then electrostatic potential energy of the system $= \frac{U}{2}$, Heat loss $= \frac{U}{2}$ and energy of each capacitor $= \frac{U}{4}$



$$C_1 = \left[\frac{2K}{K+1} \right] C$$

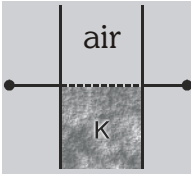

$$C_2 = \left[\frac{K+1}{2} \right] C$$

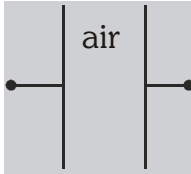

$$C_3 = C$$


When no dielectric is used

$C_2 > C_1 > C_3$



- For a given voltage, in order to store maximum energy capacitors should be connected in parallel.
- If N identical capacitors each having breakdown voltage V are joined in (i) series then the break down voltage of the combination $= NV$ (ii) parallel then the breakdown voltage of the combination $= V$
- Two capacitors are connected in series with a battery.

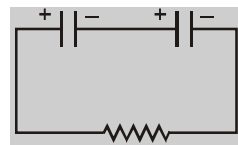Now, the battery is removed and loose wires ends are connected together then the final charge on each capacitor is zero.



- If N identical capacitors are connected then $C_{\text{series}} = \frac{C}{N}$, $C_{\text{parallel}} = NC$

Illustrations

Illustration 13.

An infinite number of capacitors of capacitance $C, 4C, 16C \dots \infty$ are connected in series then what will be their resultant capacitance ?

Solution

Let the equivalent capacitance of the combination $= C_{\text{eq}}$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C} + \frac{1}{4C} + \frac{1}{16C} + \dots \infty$$

$$= \left[1 + \frac{1}{4} + \frac{1}{16} + \dots \infty \right] \frac{1}{C}$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{1 - \frac{1}{4}} \times \frac{1}{C} \Rightarrow C_{\text{eq}} = \frac{3}{4}C$$

Illustration 14.

Three identical capacitors are connected together differently. For the same voltage applied across each combination, which one stores maximum energy ?


Solution

When all three are connected in parallel combination then this combination stores maximum energy because

$$C_{\text{eq}} \text{ will be maximum in parallel combination and } U = \frac{1}{2} C_{\text{eq}} V^2.$$

Illustration 15.

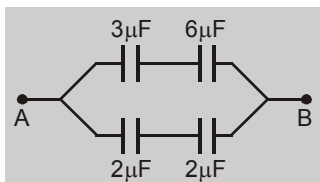What is the effective capacity between points A and B of the network of capacitors shown in figure?



Solution

$$C_1 = \frac{3 \times 6}{3 + 6} = 2 \mu\text{F}, C_2 = \frac{2}{2} = 1 \mu\text{F}$$

$$\Rightarrow C_{\text{eq}} = 2 + 1 = 3 \mu\text{F}$$

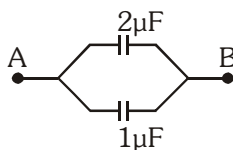
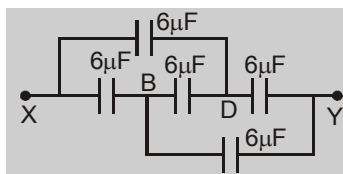
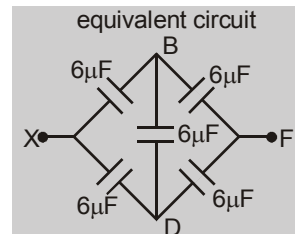


Illustration 16.


What is the effective capacitance between the points X and Y ?

**Solution**


This is a balanced Wheatstone bridge, so BD can be removed.
 $6\ \mu\text{F}$ and $6\ \mu\text{F}$ are in series so equivalent capacitance = $3\ \mu\text{F}$
 then $3\ \mu\text{F}$ and $3\ \mu\text{F}$ are in parallel so equivalent capacitance between X and Y is $6\ \mu\text{F}$.

**Illustration 17.**



What is the equivalent capacitance of the combination ?

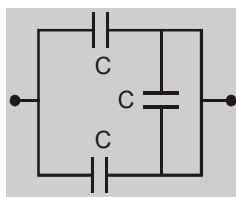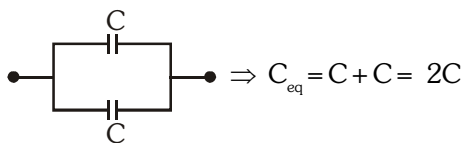**Solution**

The capacitor shown as a vertical element is shorted, so it can be removed.

**Illustration 18.**

Twelve identical capacitors each of capacitance C are connected as shown in figure.
 Find the effective capacitance between P and T.

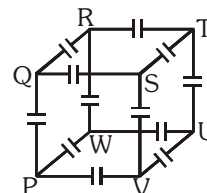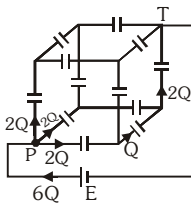Solution


$$E = \frac{2Q}{C} + \frac{Q}{C} + \frac{2Q}{C} = \frac{5Q}{C}, \quad C_{eff} = \frac{6Q}{E} = \frac{6C}{5}.$$

Illustration 19.

In Illustration 18, find the effective capacitance between P and U.

Solution

Given circuit can be redrawn as

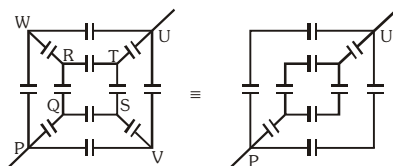


$$\text{Equivalent capacitance between P and U} = \frac{C}{3} + \frac{C}{2} + \frac{C}{2} = \frac{4C}{3}.$$



Illustration 20.

In Illustration 18, find the effective capacitance between P and V.

Solution

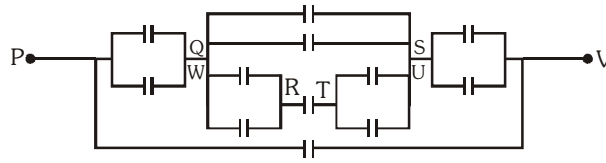


If a battery be connected across the terminals P and V, from symmetry $V_Q = V_W$ and $V_S = V_U$

$$\Rightarrow \text{Equivalent capacitance} = \frac{\left(\frac{5}{2}C\right)(C)}{\frac{5}{2}C + C} + C = \frac{12C}{7}.$$

Illustration 21.

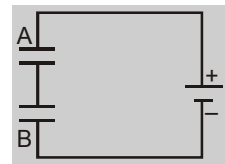Two identical capacitors A and B shown in the given circuit are joined in series with a battery. A dielectric slab of dielectric constant K is slipped between the plates of capacitor B with battery remaining connected. Then state whether the energy of capacitor A will increase or decrease?



Solution



Capacitance of capacitor B will increase so equivalent capacitance and charge on each capacitor will also increase.

We know that $U = \frac{Q^2}{2C}$, So energy of capacitor A will increase.

Illustration 22.

Six equal capacitors each of value $4 \mu\text{F}$ are connected as shown in figure.

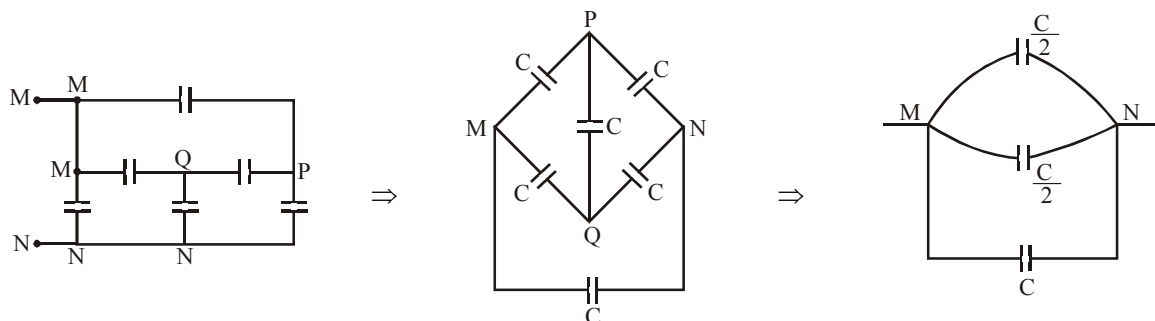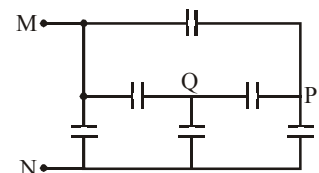Calculate the equivalent capacitance between the points M and N.




$$\Rightarrow C_{eq} = 2C = 2 \times 4 = 8 \mu\text{F}.$$



Illustration 23.

Find the equivalent capacitance of the infinite ladder shown in figure between the points A & B.

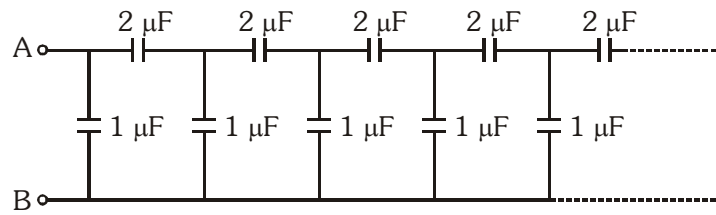**Solution**

Let equivalent capacitance be x .



$$x = \frac{2x}{2+x} + 1$$

$$x = \frac{2x+2+x}{2+x} \Rightarrow x(2+x) = 3x+2 \Rightarrow 2x+x^2 = 3x+2$$

$$\Rightarrow x^2 - x - 2 = 0$$

$$\text{Using } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{1 \pm \sqrt{1+8}}{2} = \frac{1 \pm 3}{2} = 2 \text{ and } -1$$


$$x = 2, C_{eq} = 2 \mu F \quad (\because C \neq -ve)$$

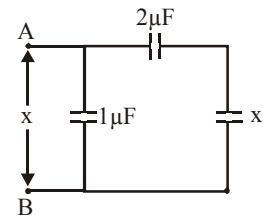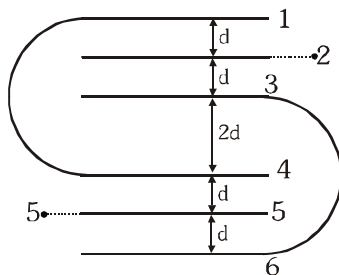**Illustration 24.**

There are six plates of equal area A and separation between the adjacent plates is d or $2d$ ($d \ll A$). They are arranged as shown in figure. Find the equivalent capacitance between points 2 and 5.

Solution

Redrawing the circuit

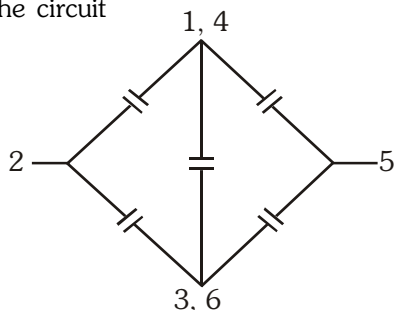

It is a wheatstone bridge with points (3, 6) and (1, 4) being equipotential. So, the capacitance $C/2$ can be removed.

$$\therefore C_{eq} = C = \frac{\epsilon_0 A}{d}$$



Illustration 25.

All capacitors given in column-I have capacitance of $1\mu\text{F}$ each.

Column-I (Circuit)		Column-II (Capacitance between X and Y)	
(A)		(P)	$\frac{3}{2}\mu\text{F}$
(B)		(Q)	$\frac{15}{8}\mu\text{F}$
(C)		(R)	$2\mu\text{F}$

Solution

(A)→(R), (B)→(Q), (C)→(P)


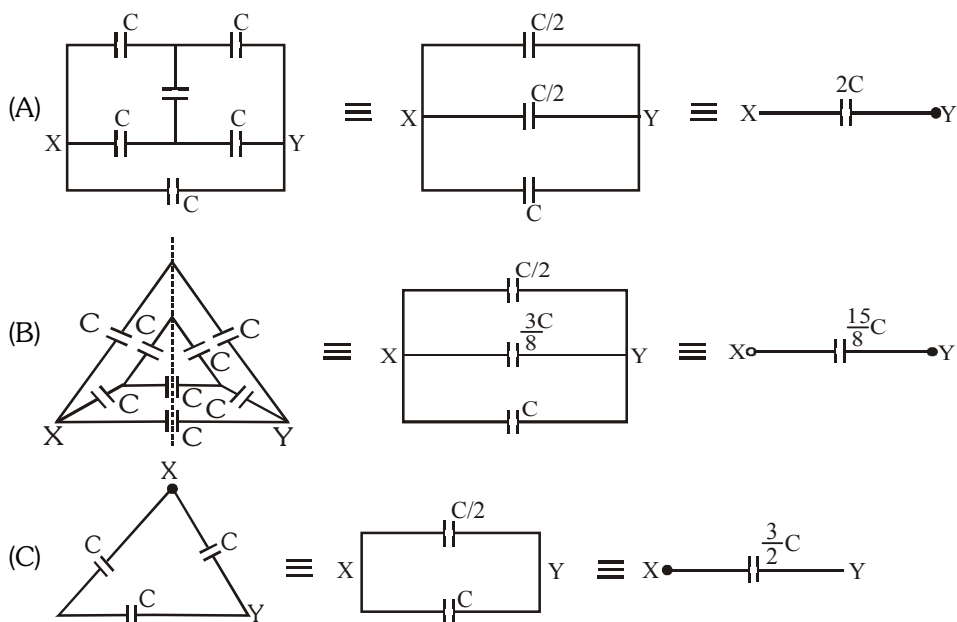


Illustration 26.

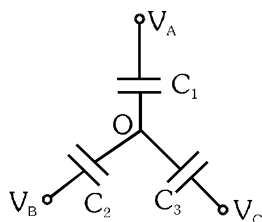Calculate the potential of point O in terms of C_1 , C_2 , C_3 , V_A , V_B , & V_C in the following circuit.



Solution


Let the potential of the junction O be V_0 . Now apply Kirchhoff's current law at a junction.

$$C_1 (V_A - V_0) + C_2 (V_B - V_0) + C_3 (V_C - V_0) = 0 \Rightarrow V_0 = \frac{C_1 V_A + C_2 V_B + C_3 V_C}{C_1 + C_2 + C_3}.$$



Illustration 27.


Four capacitors are arranged to form the given circuit. If this arrangement is connected across a voltage source then charge supplied by the source is $24 \mu\text{C}$. Calculate the charge on capacitor A.

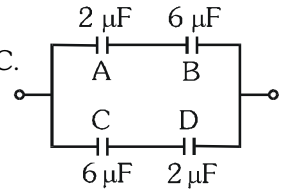**Solution**


Given circuit can be redrawn as shown in figure.

As capacitance of both the branches are same so $24 \mu\text{C}$ charge will be equally divided.

\therefore charge on capacitor A = $12 \mu\text{C}$

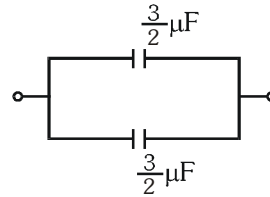**Illustration 28.**

A parallel plate capacitor with no dielectric has a capacitance of $0.5 \mu\text{F}$. Half of the space between the plates is filled with a medium of dielectric constant 2 and remaining half is filled with a medium of dielectric constant of 3 as shown in figure. Find its net capacity.

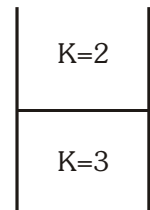**Solution**

Given that original capacitance $C = \frac{\epsilon_0 A}{d} = 0.5 \mu\text{F}$


Capacitance of part with dielectric constant 2 is $C_1 = \frac{2 \epsilon_0 A / 2}{d} = \frac{\epsilon_0 A}{d} = 0.5 \mu\text{F}$

Capacitance of part with dielectric constant 3 is $C_2 = \frac{3 \epsilon_0 A / 2}{d} = \frac{3 \epsilon_0 A}{2d} = 0.75 \mu\text{F}$


As both the capacitors are connected in parallel so $C_{eq} = C_1 + C_2 = 0.5 + 0.75 = 1.25 \mu\text{F}$

BEGINNER'S BOX-3

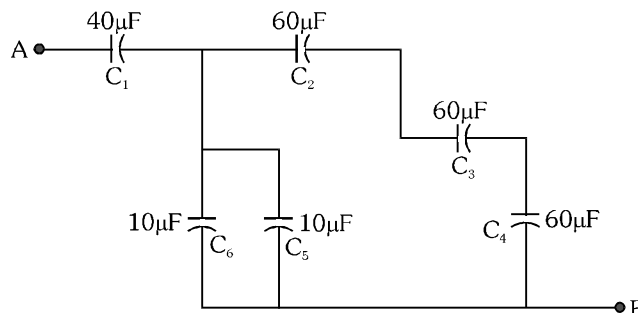- Find the equivalent capacitance of the combination of capacitors between the points A and B as shown in figure. Also calculate the total charge that flows in the circuit when a 100 V battery is connected between the points A and B



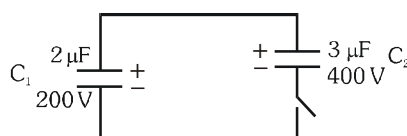- Three capacitors each of capacitance 9 pF are connected in series.
 - What is the total capacitance of the combination ?
 - What is the potential difference across each capacitor if the combination is connected to a 120 V supply?
- Two capacitors of capacity C_1 and C_2 are connected as shown in figure.




Now the switch is closed. Calculate the charge on each capacitor.




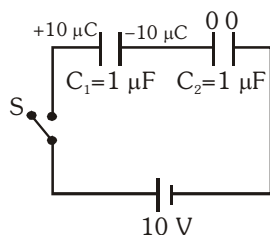Questions # 4 to 6


Following figure shows the initial charges on the capacitors. After the switch S is closed, find -



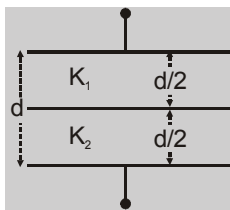
4. The charge on capacitor C_1
 (A) $0 \mu\text{C}$ (B) $5 \mu\text{C}$ (C) $10 \mu\text{C}$ (D) None of these
5. The charge on capacitor C_2
 (A) $0 \mu\text{C}$ (B) $5 \mu\text{C}$ (C) $10 \mu\text{C}$ (D) None of these
6. The work done by the battery
 (A) $50 \mu\text{J}$ (B) $100 \mu\text{J}$ (C) $150 \mu\text{J}$ (D) Zero
7. Two dielectric slabs of dielectric constants K_1 and K_2 have been inserted in between the plates of a capacitor as shown below. What will be the capacitance of the capacitor inserted ?
 (Plate area = A)



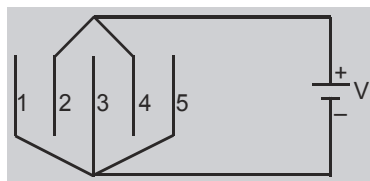8. Five identical plates each of area A are joined as shown in the figure. The distance between successive plates is d. The plates are connected to potential difference of V volt. Find the charges of plates 1 and 4








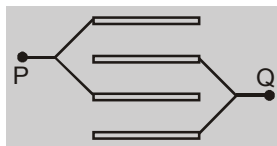9. Four plates of the same area A are joined as shown in the figure. The distance between successive plates is d. Find the equivalent capacity across PQ will be



10. Two identical capacitors each of capacity C are charged upto same potential V. Now their oppositely charged plates are connected together then calculate the -
 - (a) energy of each capacitor before connection.
 - (b) potential of each capacitor after connection.
 - (c) charge of each capacitor after connection.
 - (d) energy stored in each capacitor after connection.
 - (e) energy loss in the form of heat.

10. CHARGING & DISCHARGING OF A CONDENSER

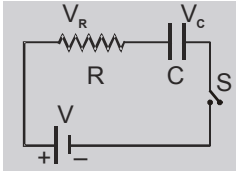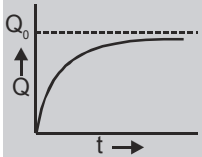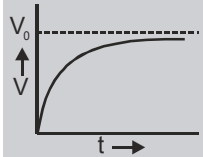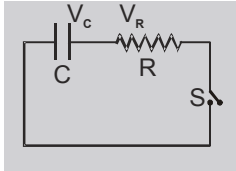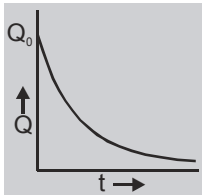
Charging	Discharging
<ul style="list-style-type: none"> When a capacitor, resistance and battery are connected in series and key is closed.  $V = V_C + V_R$ $V = \frac{Q}{C} + IR = \frac{Q}{C} + \frac{dQ}{dt}R$ $R \frac{dQ}{dt} = \frac{CV - Q}{C} \Rightarrow \int_0^Q \frac{dQ}{CV - Q} = \int_0^t \frac{dt}{CR}$ $-\ln \frac{CV - Q}{CV} = \frac{t}{CR} \Rightarrow 1 - \frac{Q}{CV} = e^{-t/RC}$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $Q = CV[1 - e^{-t/RC}]$ </div> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $Q = Q_0[1 - e^{-t/RC}]$ </div> <p>This is the charge at any instant t.</p> <ul style="list-style-type: none"> t = RC is known as time constant. At the end of one time constant the charge on the capacitor rises to 63% of its maximum value. Potential diff. across the condenser plates at any instant is $V = V_0(1 - e^{-t/RC})$ <div style="display: flex; justify-content: space-around;">   </div>	<ul style="list-style-type: none"> When a charged capacitor, resistance and key are connected in series and key is closed, then energy stored in the capacitor is used to drive current in the circuit.  $V_C + V_R = 0$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $V = V_0 e^{-t/RC}$ </div> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $Q = Q_0 e^{-t/RC}$ </div> <p>This is the quantity of charge & voltage at any instant t.</p> <ul style="list-style-type: none"> At t = RC the charge falls to 37% of its maximum initial value. <div style="display: flex; justify-content: space-around;">  </div>

11. VAN DE GRAAFF GENERATOR (Only for 12th Board)

- (i) It uses a moving belt to buildup very high amounts of electrical potential (of the order of ten million volts) on a hollow metal globe on the top of a stand.
- (ii) This machine acts on the principle of corona discharge.
- (iii) It is based on the following principles
 - Action of sharp points : charges are leaked from pointed ends of charged conductors. This creates an electric wind (as moving air is ionized) which moves away from the conductor.
 - The property that the charge given to a hollow conductor is transferred to the outer surface and is distributed uniformly on it.



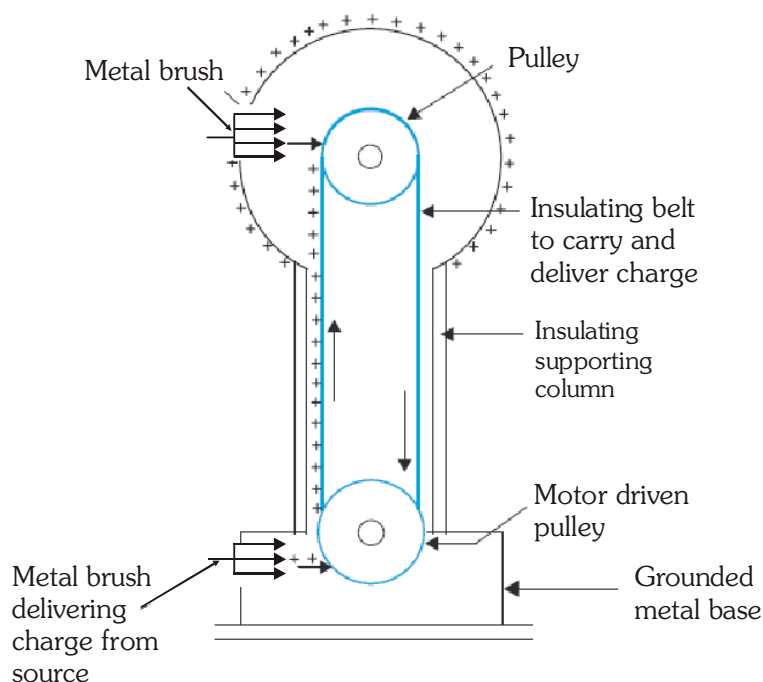
- (iv) A Van de Graaff generator operates by transferring electric charge from a moving belt to a terminal
- (v) The potential at the outer surface would also keep rising, at least until we reach the break down field of air, which is about $3 \times 10^6 \text{ V/m}$.
- (vi) It is a source of high voltage for accelerating charge particles to a high speed.



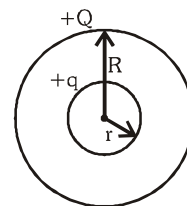- (vii) Consider a shell of radius R and having a charge Q enclosing a smaller sphere of radius r and having a charge q . The potential of the two spheres are

$$V(R) = \frac{1}{4\pi\epsilon_0} \left(\frac{Q}{R} + \frac{q}{R} \right)$$

and
$$V(r) = \frac{1}{4\pi\epsilon_0} \left(\frac{Q}{R} + \frac{q}{r} \right)$$



The potential difference between the inner and outer sphere is $V(r) - V(R) = \frac{q}{4\pi\epsilon_0} \left[\frac{1}{r} - \frac{1}{R} \right]$ thus for positive q , whatever be the magnitude and sign of Q , the small sphere is at a higher potential than the shell. When an electrical contact is established, charge would flow from the small sphere to the shell.

Illustrations

Illustration 29.

In the given circuit calculate the potential difference across the $2 \mu\text{F}$ capacitor in the steady state condition, if internal resistance of battery is 1 ohm .

Solution

Current in the steady state condition $= \frac{4}{2+1+1} = 1 \text{ A}$

Potential difference between x and $y = 3 \text{ V}$.

Divide this 3V in inverse ratio of capacity

Voltage on $2 \mu\text{F}$ capacitor $= \frac{1}{2+1} \times 3 = 1\text{V}$.

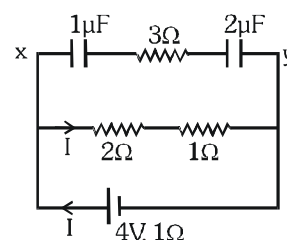
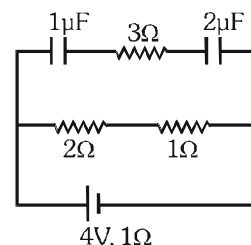
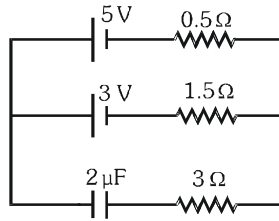


Illustration 30.

In the given circuit find the charge on the capacitor.


**Solution**

In the steady state no current is there in capacitors's branch.

$$\text{So current } I = \frac{2}{0.5 + 1.5} = 1\text{A}$$


$$\text{Voltage across capacitor } V_C = 3 + 1.5 \times 1 = 4.5\text{ V}$$

$$\Rightarrow Q = CV_C = 2 \times 10^{-6} \times 4.5 = 9 \times 10^{-6}\text{ C}$$

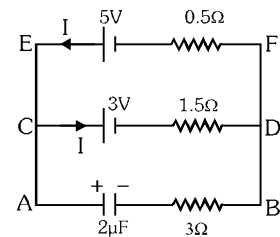**Illustration 31.**


In the given circuit find the :-

- initial current supplied by the battery.
- final current supplied by the battery.

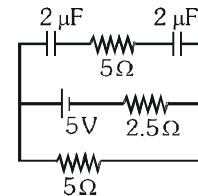**Solution**

- Initially capacitor behaves just like a zero resistance wire
Total resistance $R = 5\Omega$


$$I = \frac{5}{5} = 1\text{A}$$

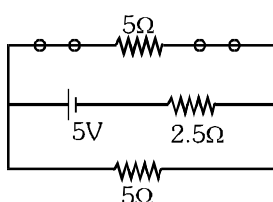

- Finally it behaves as open circuit resistance wire

$$\text{Total resistance } R = 7.5\Omega$$

$$I = \frac{5}{7.5} = \frac{2}{3}\text{ A}$$

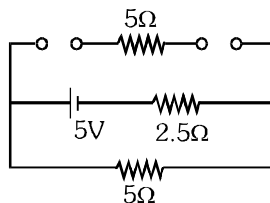**Illustration 32.**

Calculate the charge on each capacitor in the steady state .

Solution


When capacitor is fully charged, no current will flow through it

$$\therefore \text{ current in the circuit will be } I = \frac{10}{1+4} = 2\text{ A}$$

$$\therefore \text{ voltage drop across } 4\Omega \text{ resistance is } V = IR = 2 \times 4 = 8\text{ V.}$$

This voltage will get divided between the two capacitors. So voltage across each capacitor is $V_C = 4\text{V}$

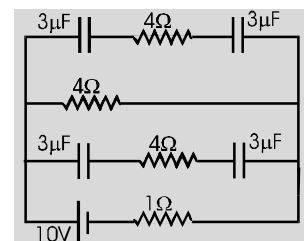
$$\therefore \text{ charge on each capacitor } Q = CV = 4 \times 3 \times 10^{-6}\text{ C} = 12\text{ }\mu\text{C}$$




BEGINNER'S BOX-4

1. Figure shows, the graph of the current in a discharging circuit of a capacitor through a resistor of resistance $10\ \Omega$:





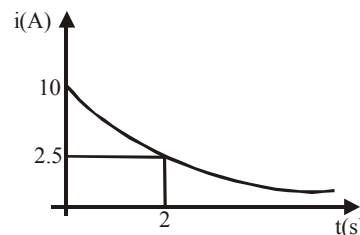
- (i) Find the initial potential difference across the capacitor.
- (ii) Find the capacitance of the capacitor.
- (iii) Find the total heat produced in the circuit.
- (iv) Find the time constant of the circuit.



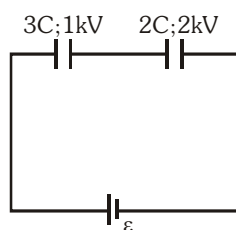
2. The diagram shows two capacitors with capacitance and breakdown voltages as mentioned. What should be the maximum value of the external emf source such that no capacitor undergoes breakdown?



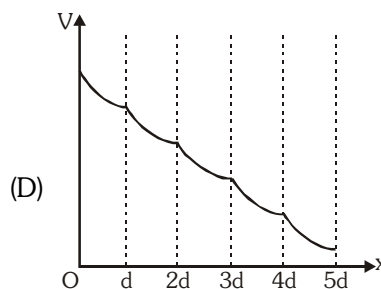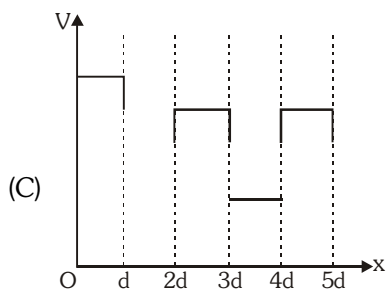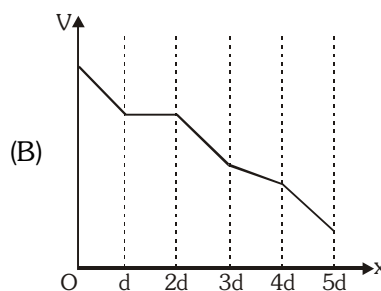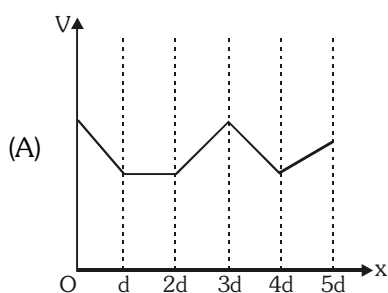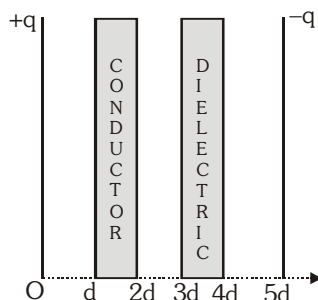- (A) 2.5 kV (B) $10/3$ kV (C) 3 kV (D) 1 kV
3. The distance between plates of a parallel plate capacitor is $5d$. The positively charged plate is at $x=0$ and negatively charged plates is at $x=5d$. Two slabs – one of conductor and the other of a dielectric, both of same thickness d are inserted between the plates as shown in figure. Potential (V) versus distance x graph will be



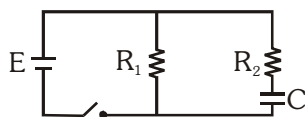4. A $400 \mu\text{F}$ condenser is charged at the steady rate of $100 \mu\text{C}$ per second. Calculate the time required to establish a potential difference of 100 volts between its plates.
5. For the circuit shown in figure, find



- (a) the initial currents through each resistor after the switch is closed.
- (b) steady state currents through each resistor after the switch is closed.
- (c) final energy stored in the capacitor after the switch is closed.
- (d) time constant of the circuit when switch is opened.
- (e) time constant of the circuit when switch is closed.
6. A condenser of capacitance $2 \mu\text{F}$ has been charged to 200 V. It is now discharged through a resistance; the heat produced in the wire is

ANSWERS

BEGINNER'S BOX-1

1. Zero 2. Zero, $\frac{1}{2} \frac{Q^2}{C}$
3. 4W 4. 2 times
5. 3 m 6. $3.2 \times 10^{-4} \text{ F}$
7. $C_A > C_B$ 8. 0.09 C, 135 J
9. $\sqrt{\frac{C_2}{C_1}}$

BEGINNER'S BOX-2

1. $\frac{\epsilon_0 AV^2}{2d}$ 2. A
3. 3.5 4. $4.3 \times 10^{-9} \text{ J}$
5. B 6. $5C_0, W_0/5$
7. 10^{-3} m^2 8. $200 \mu\text{C}; 800 \mu\text{C}$
9. $400 \mu\text{C}$ 10. $\frac{1}{2} \epsilon_0 \frac{V^2}{d^2}$
11. $\sigma_{\text{Big}} = 4\sigma_{\text{Small}}$

BEGINNER'S BOX-3

1. $20 \mu\text{F}; 2 \times 10^{-3} \text{ C}$ 2. (a) 3 pF; (b) 40 V
3. $640 \mu\text{C}; 960 \mu\text{C}$ 4. (C) 5. (A)
6. (D) 7. $\frac{2\epsilon_0 A}{d} \left(\frac{K_1 K_2}{K_1 + K_2} \right)$
8. $\frac{-\epsilon_0 AV}{d}, \frac{2\epsilon_0 AV}{d}$ 9. $\frac{3\epsilon_0 A}{d}$
10. (a) $\frac{1}{2} CV^2$ (b) Zero; (c) Zero & Zero;
(d) Zero & Zero; (e) CV^2


BEGINNER'S BOX-4

1. (i) 100 volts ; (ii) $\frac{1}{10 \ln 2} \text{ F}$;
- (iii) $\frac{500}{\ln 2} \text{ joules}$; (iv) $\frac{1}{\ln 2} \text{ seconds}$
2. (A) 3. (B) 4. 400 s
5. (a) $i_1 = \frac{E}{R_1}$ and $i_2 = \frac{E}{R_2}$; (b) $i_1 = \frac{E}{R_1}, i_2 = 0$;
- (c) $U = \frac{1}{2} CE^2$; (d) $C(R_1 + R_2)$; (e) $\tau = R_2 C$
6. 0.04 J



EXERCISE-I (Conceptual Questions)

CAPACITANCE, ENERGY STORED IN CAPACITOR & SPHERICAL CAPACITOR

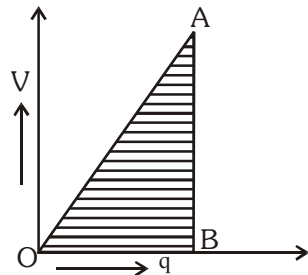- The capacitance C of a capacitor is :-
 - independent of the charge and potential of the capacitor.
 - dependent on the charge and independent of potential.
 - independent of the geometrical configuration of the capacitor.
 - independent of the dielectric medium between the two conducting surfaces of the capacitor.
- To increase the charge on the plate of a capacitor implies to :-
 - decrease the potential difference between the plates.
 - decrease the capacitance of the capacitor.
 - increase the capacitance of the capacitor.
 - increase the potential difference between the plates.
- The net charge on a capacitor is :-
 - $2q$
 - $q/2$
 - 0
 - infinity
- The earth has Volume ' V ' and Surface area ' A '; then its capacitance would be :
 - $4\pi\epsilon_0 \frac{A}{V}$
 - $4\pi\epsilon_0 \frac{V}{A}$
 - $12\pi\epsilon_0 \frac{V}{A}$
 - $12\pi\epsilon_0 \frac{A}{V}$
- Capacitors are used in electrical circuits where appliances need rapid :
 - Current
 - Voltage
 - Watt
 - Resistance
- Which of the following is called electrical energy tank ?
 - Resistor
 - Inductance
 - Capacitor
 - Motor
- If the maximum circumference of a sphere is 2 m, then its capacitance in water would be :-
(Dielectric constant of water = 81)
 - 27.65 pF
 - 2385 pF
 - 236.5 pF
 - 2865 pF
- The two parallel plates of a condenser have been connected to a battery of 300 V and the charge collected at each plate is 1 μC . The energy supplied by the battery is :
 - $6 \times 10^{-4}\text{J}$
 - $3 \times 10^{-4}\text{J}$
 - $1.5 \times 10^{-4}\text{J}$
 - $4.5 \times 10^{-4}\text{J}$
- When a capacitor of value 200 μF charged to 200V is discharged separately through resistance of 2 ohms and 8 ohms, then heat produced in joule will respectively be:
 - 4 and 16
 - 16 and 4
 - 4 and 8
 - 4 and 4
- The potential to which a conductor is raised, depends on :-
 - the amount of charge
 - the geometry and size of the conductor
 - both (1) and (2)
 - None of these
- The charge q on a capacitor varies with voltage as shown in figure. The area of the triangle AOB represents :
 - electric field between the plates
 - electric flux between the plates
 - energy density
 - energy stored by the capacitor.
- An uncharged capacitor is connected to a battery. On charging the capacitor :-
 - all the energy supplied is stored in the capacitor.
 - half the energy supplied is stored in the capacitor.
 - the energy stored depends upon the capacity of the capacitor only.
 - the energy stored depends upon the time for which the capacitor is charged.



CYLINDRICAL CAPACITOR PARALLEL PLATE CAPACITOR & EFFECT OF DIELECTRIC SLAB


13. The capacity of parallel plate condenser depends on :
- (1) the type of metal used
 - (2) the thickness of plates
 - (3) the potential difference applied across the plates
 - (4) the separation between the plates.

14. A parallel plate capacitor has rectangular plates of 400 cm^2 area and are separated by a distance of 2 mm with air as the medium. What charge will appear on the plates if a 200 volt potential difference is applied across the capacitor ?

- (1) $3.54 \times 10^{-6} \text{ C}$
- (2) $3.54 \times 10^{-8} \text{ C}$
- (3) $3.54 \times 10^{-10} \text{ C}$
- (4) $1770.8 \times 10^{-13} \text{ C}$

15. There are two metallic plates of a parallel plate capacitor. One plate is given a charge $+q$ while the other is earthed as shown. Points P, P_1 and P_2 are taken as shown in adjoining figure. Then the electric intensity is not zero at :

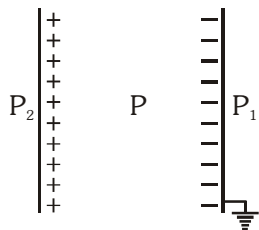- (1) P only
- (2) P_1 only
- (3) P_2 only
- (4) P, P_1 and P_2



16. The distance between the plates of a circular parallel plate capacitor of diameter 40 mm, whose capacity is equal to that of a metallic sphere of radius 1m will be :

- (1) 0.01 mm
- (2) 0.1 mm
- (3) 1.0 mm
- (4) 10 mm

17. The energy density in a parallel plate capacitor is given as $2.1 \times 10^{-9} \text{ J/m}^3$. The value of the electric field in the region between the plates is :

- (1) 2.1 NC^{-1}
- (2) 21.6 NC^{-1}
- (3) 72 NC^{-1}
- (4) 8.4 NC^{-1}

18. A charged parallel plate capacitor of distance (d) has U_0 energy. A slab of dielectric constant (K) and thickness (d) is then introduced between the plates of the capacitor. The new energy of the system is given by :

- (1) KU_0
- (2) K^2U_0
- (3) $\frac{U_0}{K}$
- (4) $\frac{U_0}{K^2}$

19. The energy and capacity of a charged parallel plate capacitor are U and C respectively. Now a dielectric slab of $\epsilon_r = 6$ is inserted in it then energy and capacity becomes : (Assuming charge on plates remains constant)

- (1) $6U, 6C$
- (2) U, C
- (3) $\frac{U}{6}, 6C$
- (4) $U, 6C$

20. Distance between the plates of a parallel plate capacitor is 'd' and area of each plate is A. When a slab of dielectric constant K and thickness t is placed between the plates, its capacity becomes:

- (1) $\frac{\epsilon_0 A}{\left[d + t \left\{ 1 - \frac{1}{K} \right\} \right]}$
- (2) $\frac{\epsilon_0 A}{\left[d + t \left\{ 1 + \frac{1}{K} \right\} \right]}$
- (3) $\frac{\epsilon_0 A}{\left[d - t \left\{ 1 + \frac{1}{K} \right\} \right]}$
- (4) $\frac{\epsilon_0 A}{\left[d - t \left\{ 1 - \frac{1}{K} \right\} \right]}$

21. When a slab of dielectric medium is placed between the plates of a parallel plate capacitor which is connected with a battery, then the charge on plates in comparison with earlier charge :

- (1) is less
- (2) is same
- (3) is more
- (4) depends on the nature of the material inserted

22. A glass slab is put within the plates of a charged parallel plate condenser. Which of the following quantities does not change ?

- (1) energy of the condenser
- (2) capacity
- (3) intensity of electric field
- (4) charge

23. A parallel plate capacitor is connected to a battery and a dielectric slab is inserted between the plates, then which quantity increase :

- (1) potential difference
- (2) electric field
- (3) stored energy
- (4) E.M.F. of battery



24. A parallel plate capacitor is charged by a battery. After charging the capacitor, battery is disconnected and a dielectric plate is inserted between the plates. Then which of the following statements is not correct there is a/an ?

(1) increase in the stored energy
(2) decrease in the potential difference
(3) decrease in the electric field
(4) increase in the capacitance

25. A parallel plate capacitor is charged by a battery. After charging the capacitor, battery is disconnected and distance between the plates is decreased then which of the following statement is correct ?

(1) electric field does not remain constant
(2) potential difference is increased
(3) the capacitance decreases
(4) the stored energy decreases

26. A parallel plate capacitor is connected with a battery whose potential difference remains constant. If the plates of the capacitor are shifted apart then the intensity of electric field :

(1) decreases and charge on plates also decreases.
(2) remains constant but charge on plates decreases.
(3) remains constant but charge on the plates increases.
(4) increases but charge on the plates decreases.


27. A parallel plate capacitor is charged with a battery and afterwards the battery is removed. if now, with the help of insulating handles, the distance between the plates is increased, then

(1) charge on capacitor increases and capacity decreases.
(2) potential difference between the plates increases.
(3) capacity of capacitor increases.
(4) value of energy stored in capacitor decreases.

28. Can a metal be used as a medium for dielectric ?

(1) Yes
(2) No
(3) Depends on its shape
(4) Depends on dielectric

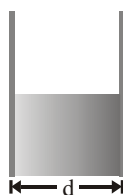
29. A parallel plate air capacitor has a capacitance C . When it is half filled with a dielectric of dielectric constant 5, the percentage increase in the capacitance will be :-



(1) 400% (2) 66.6% (3) 33.3% (4) 200%


COMBINATION OF CAPACITORS & SHARING OF CHARGES

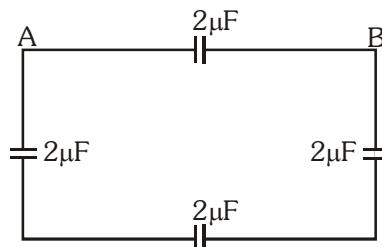30. The equivalent capacitance between the points A and B in the given diagram is :



(1) $8 \mu\text{F}$ (2) $6 \mu\text{F}$
(3) $\frac{8}{3} \mu\text{F}$ (4) $\frac{3}{8} \mu\text{F}$

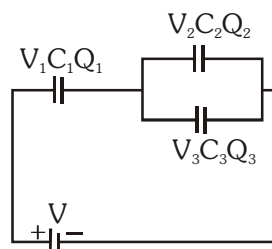31. In an adjoining figure three capacitors C_1 , C_2 and C_3 are joined to a battery. The correct condition will be :



(1) $Q_1 = Q_2 = Q_3$ and $V_1 = V_2 = V_3 = V$
(2) $Q_1 = Q_2 + Q_3$ and $V = V_1 + V_2 + V_3$
(3) $Q_1 = Q_2 + Q_3$ and $V = V_1 + V_2$
(4) $Q_2 = Q_3$ and $V_2 = V_3$


(Symbols have their usual meanings)

32. A number of capacitors, each of capacitance $1 \mu\text{F}$ and each one of which gets punctured if a potential difference just exceeding 500 volt is applied, are provided. Then an arrangement suitable for giving a capacitor of capacitance $3 \mu\text{F}$ across which 2000 volt may be applied requires at least :

(1) 4 component capacitors
(2) 12 component capacitors
(3) 48 component capacitors
(4) 16 component capacitors



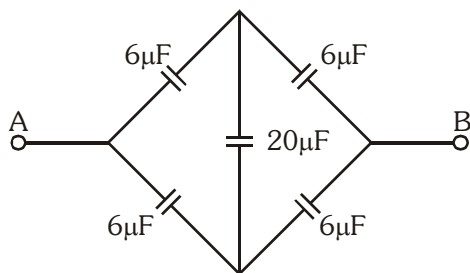33. The effective capacity of the network between terminals A and B is :




- (1) $6 \mu\text{F}$ (2) $20 \mu\text{F}$
(3) $3 \mu\text{F}$ (4) $10 \mu\text{F}$

34. A series combination of two capacitances of value $0.1 \mu\text{F}$ and $1 \mu\text{F}$ is connected with a source of voltage 500 volts. The potential difference in volts across the capacitor of value $0.1 \mu\text{F}$ will be :


- (1) 50 (2) 500
(3) 45.5 (4) 454.5

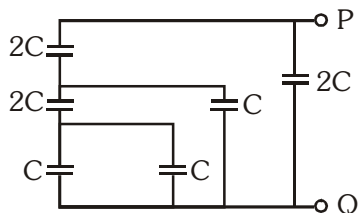35. The value of equivalent capacitance of the combination shown in figure, between the points P and Q is :




- (1) $3C$
(2) $2C$
(3) C
(4) $C/3$

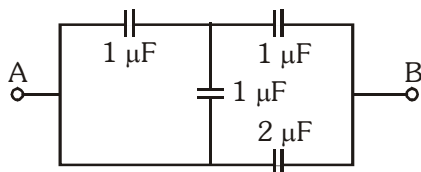36. The equivalent capacitance between points A and B of the circuit shown will be :



- (1) $\frac{2}{3} \mu\text{F}$ (2) $\frac{5}{3} \mu\text{F}$
(3) $\frac{8}{3} \mu\text{F}$ (4) $\frac{7}{3} \mu\text{F}$

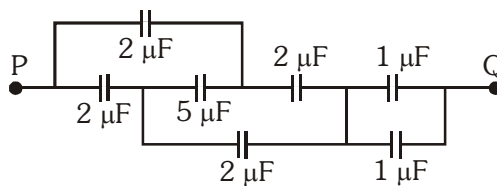37. The effective capacitance between the points P and Q of the arrangement shown in the figure is :



- (1) $(1/2) \mu\text{F}$ (2) $1 \mu\text{F}$
(3) $2 \mu\text{F}$ (4) $1.33 \mu\text{F}$

38. Two spheres of radii R_1 and R_2 having equal charges are joined together with a copper wire. If V is the potential of each sphere after they are separated from each other, then the initial charge on both spheres was :

- (1) $\frac{V}{k}(R_1 + R_2)$ (2) $\frac{V}{2k}(R_1 + R_2)$
(3) $\frac{V}{3k}(R_1 + R_2)$ (4) $\frac{V}{k} \frac{(R_1 R_2)}{(R_1 + R_2)}$

39. Two spheres of radii 1 cm and 2 cm have been charged with 1.5×10^{-8} and 0.3×10^{-7} coulombs of positive charge. When they are connected with a wire, charge :

- (1) will flow from the first to the second
(2) will flow from the second to the first
(3) will not flow at all
(4) may flow either from first to second, or from the second to first, depending upon the length of the connecting wire

40. Half of the space between a parallel plate capacitor is filled with a medium of dielectric constant K parallel to the plates. If initially the capacity was C , then the new capacity will be :


- (1) $2KC/(1+K)$ (2) $C(K+1)/2$
(3) $CK/(1+K)$ (4) KC

41. Two identical parallel plate capacitors are connected in series and then joined with a battery of 100 V. A sheet of dielectric constant 4.0 is inserted between the plates of second capacitor. The potential difference across the capacitors will be respectively :

- (1) 50 V, 50 V (2) 80 V, 20 V
(3) 20 V, 80 V (4) 75 V, 25 V




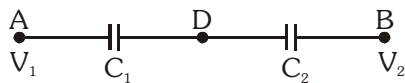42. Two capacitances C_1 and C_2 in a circuit are joined as shown in figure. The potential of point A is V_1 and that of B is V_2 . The potential of point D will be :




- (1) $\frac{1}{2} (V_1 + V_2)$ (2) $\frac{C_2 V_1 + C_1 V_2}{C_1 + C_2}$
 (3) $\frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$ (4) $\frac{C_2 V_1 - C_1 V_2}{C_1 + C_2}$

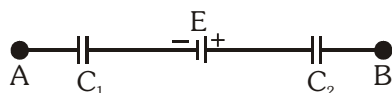43. A circuit has a section AB as shown in the figure with $E = 10$ V, $C_1 = 1.0$ μ F, $C_2 = 2.0$ μ F and the potential difference $V_A - V_B = 5$ V. The voltage across C_1 is :



- (1) zero
 (2) 5 V
 (3) 10 V
 (4) 15 V

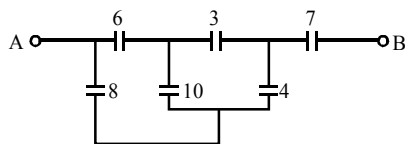44. In the circuit diagram shown all the capacitors are in mF. The equivalent capacitance between points A & B is (in mF) :




- (1) 14/5 (2) 7.5
 (3) 3/7 (4) None of these

45. Two capacitances C_1 and C_2 are connected in series; assume that $C_1 < C_2$. The equivalent capacitance of this arrangement is C , where :

- (1) $C < C_1/2$ (2) $C_1/2 < C < C_1$
 (3) $C_1 < C < C_2$ (4) $C_2 < C < 2C_2$

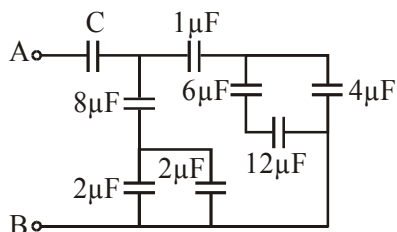
46. In the following circuit the resultant capacitance between A & B is 1μ F. Find the value of C :



- (1) $\frac{23}{32} \mu$ F (2) $\frac{32}{23} \mu$ F (3) $\frac{13}{23} \mu$ F (4) $\frac{23}{13} \mu$ F


CHARGING AND DISCHARGING OF CAPACITORS & CAPACITOR'S CIRCUIT

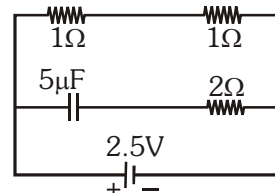47. A capacitor of capacitance 5μ F is connected as shown in the figure. The internal resistance of the cell is 0.5Ω . The amount of charge on the capacitor plate is :




- (1) 0
 (2) 5μ C
 (3) 10μ C
 (4) 25μ C

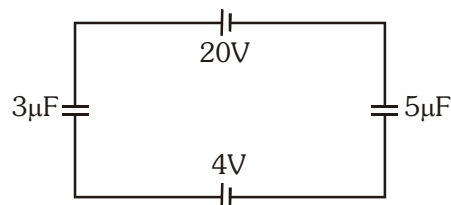48. In the given circuit, the potential difference across 3μ F capacitor will be :




- (1) 16 V (2) 10 V
 (3) 6 V (4) 4 V

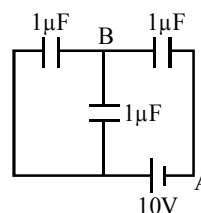49. If potential of A is 10 V, then potential of B is :



- (1) $25/3$ V (2) $50/3$ V
 (3) $100/3$ V (4) 50 V

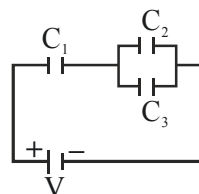
50. Capacitance $C_1 = 2C_2 = 2C_3$ and potential difference across C_1 , C_2 and C_3 are V_1 , V_2 and V_3 respectively then :



- (1) $V_1 = V_2 = V_3$
 (2) $V_1 = 2V_2 = 2V_3$
 (3) $2V_1 = V_2 = V_3$
 (4) $2V_1 = 2V_2 = V_3$




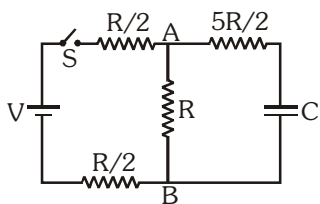51. In the circuit shown in figure, the battery is an ideal one with emf V . The capacitor is initially uncharged. Switch S is closed at time $t = 0$.




The final charge Q on the capacitor is :

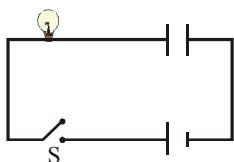- (1) $\frac{CV}{2}$ (2) $\frac{CV}{3}$
 (3) CV (4) $\frac{CV}{6}$
52. In previous question, what is the current in the steady state is ?
- (1) $\frac{V}{2R}$ (2) $\frac{V}{R}$
 (3) $\frac{2V}{R}$ (4) $\frac{V}{3R}$
53. A bulb, a capacitor and a battery are connected together as shown here, with switch S initially open. When the switch S is closed, which one of the following is true ?



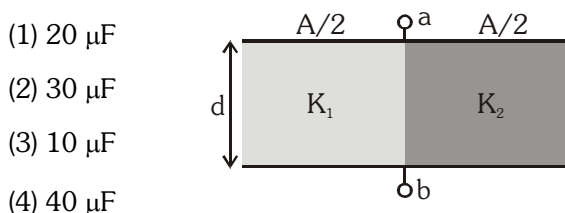- (1) The bulb will light up for an instant when the capacitor starts charging.
 (2) The bulb will light up when the capacitor is fully charged
 (3) The bulb will not light up at all
 (4) The bulb will light up and go off at regular intervals.
54. The capacity of a parallel plate air capacitor is $10 \mu\text{F}$. As shown in the figure this capacitor is divided into two equal parts; these parts are filled by media of dielectric constants $K_1=2$ and $K_2=4$. Capacity of this arrangement will be :



55. Three capacitors, each of value $1 \mu\text{F}$ are so combined that the resultant capacity is $1.5 \mu\text{F}$. Then :

- (1) All three capacitors are connected in parallel.
 (2) All three capacitors are connected in series.
 (3) Third capacitor is in series with a parallel combination of the other two.
 (4) Third capacitor is in parallel with a series combination of the other two.

56. Two conducting spheres of radii R_1 and R_2 are charged with charges Q_1 and Q_2 respectively. On bringing them in contact there is :

- (1) no change in the energy of the system
 (2) an increase in the energy of the system if $Q_1 R_2 \neq Q_2 R_1$
 (3) always a decrease in the energy of the system
 (4) a decrease in the energy of the system if $Q_1 R_2 \neq Q_2 R_1$


57. A capacitor is charged with a battery and energy stored is U . After disconnecting the battery another capacitor of same capacity is connected in parallel with it. The energy stored in each capacitor is:

- (1) $U/2$ (2) $U/4$ (3) $4U$ (4) $2U$

58. Three capacitors of capacitances $3 \mu\text{F}$, $10 \mu\text{F}$ and $15 \mu\text{F}$ are connected in series to a voltage source of 100 V . The charge on $15 \mu\text{F}$ is :

- (1) $50 \mu\text{C}$ (2) $160 \mu\text{C}$
 (3) $200 \mu\text{C}$ (4) $280 \mu\text{C}$

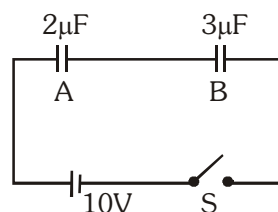59. Two capacitors A and B are connected in series with a battery as shown in the figure. When the switch S is closed and the two capacitors get charged fully, then :




- (1) the potential difference across the plates of A is 4 V and across the plates of B is 6 V
 (2) the p.d. across the plates of A is 6 V and across the plates of B is 4 V
 (3) the ratio of electrical energies stored in A and B is $2 : 3$
 (4) the ratio of charges on A and B is $3 : 2$



60. An automobile spring extends 0.2 m for 5000 N load. The ratio of potential energy stored in this spring when it has been compressed by 0.2 m to the potential energy stored in a $10 \mu\text{F}$ capacitor at a potential difference of 10000 V will be :

(1) $\frac{1}{4}$ (2) 1 (3) $\frac{1}{2}$ (4) 2

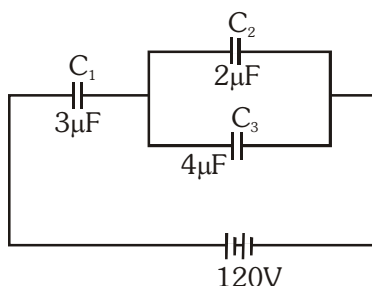61. The charge on each capacitors shown in figure and the potential difference across them will be respectively :-



- (1) $240 \mu\text{C}$, $80 \mu\text{C}$, $160 \mu\text{C}$ and 80 V, 40 V, 40 V
 (2) $300 \mu\text{C}$, $75 \mu\text{C}$, $150 \mu\text{C}$ and 40 V, 80 V, 60 V
 (3) $220 \mu\text{C}$, $70 \mu\text{C}$, $140 \mu\text{C}$ and 60 V, 50 V, 40 V
 (4) none of these

62. Three capacitance $2 \mu\text{F}$, $3 \mu\text{F}$ and $6 \mu\text{F}$ are connected in series with a 10 volt battery, then charge on $3 \mu\text{F}$ capacitor is :

(1) $5 \mu\text{C}$ (2) $10 \mu\text{C}$
 (3) $11 \mu\text{C}$ (4) $15 \mu\text{C}$

63. Two charged spheres having radii a and b are joined with a wire then the ratio of electric field E_a/E_b on their respective surfaces is :

(1) a/b (2) b/a
 (3) a^2/b^2 (4) b^2/a^2

64. A solid conducting sphere of radius R_1 is surrounded by another concentric hollow conducting sphere of radius R_2 . The capacitance of this assembly is proportional to :

(1) $\frac{R_2 - R_1}{R_1 R_2}$ (2) $\frac{R_2 + R_1}{R_1 R_2}$
 (3) $\frac{R_1 R_2}{R_1 + R_2}$ (4) $\frac{R_1 R_2}{R_2 - R_1}$

65. Two spherical conductors A and B of radius a and b ($b > a$) are placed in air concentrically. B is given a charge $+Q$ coulombs and A is grounded. The equivalent capacitance of these is :

(1) $4\pi\epsilon_0 \frac{ab}{(b-a)}$ (2) $4\pi\epsilon_0 (a+b)$
 (3) $4\pi\epsilon_0 b$ (4) $4\pi\epsilon_0 \frac{b^2}{(b-a)}$

66. Time constant of a series R-C circuit is :-

(1) $+RC$ (2) $-RC$
 (3) $\frac{R}{C}$ (4) $\frac{C}{R}$

67. Energy per unit volume for a capacitor having area A and separation d kept at potential difference V is given by :

(1) $\frac{1}{2} \epsilon_0 \frac{V^2}{d^2}$ (2) $\frac{1}{2} \epsilon_0 \frac{V^2}{d^2}$
 (3) $\frac{\epsilon_0 V^2 A^2}{2d^2}$ (4) $\frac{1}{2} \frac{V^2 A^2}{\epsilon_0 d^2}$


68. A capacitor of capacity C_1 charged upto a voltage V and then connected to an uncharged capacitor of capacity C_2 . Then final potential difference across each will be :

(1) $\frac{C_2 V}{C_1 + C_2}$ (2) $\frac{C_1 V}{C_1 + C_2}$
 (3) $\left(1 + \frac{C_2}{C_1}\right) V$ (4) $\left(1 - \frac{C_2}{C_1}\right) V$

69. A conducting sphere of radius 10 cm is charged with $10 \mu\text{C}$. Another uncharged sphere of radius 20 cm is allowed to touch it for some time. After that, if the spheres are separated, then surface density of charge on the spheres will be in the ratio of :

(1) 1 : 4 (2) 1 : 3 (3) 2 : 1 (4) 1 : 1

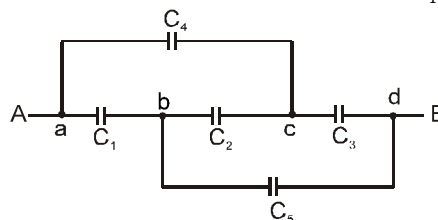70. In the given figure, the capacitors C_1 , C_3 , C_4 , C_5



have a capacitance $4 \mu\text{F}$ each. If the capacitor C_2 has a capacitance $10 \mu\text{F}$, then effective capacitance between A and B will be :

(1) $2 \mu\text{F}$ (2) $4 \mu\text{F}$ (3) $6 \mu\text{F}$ (4) $8 \mu\text{F}$



71. Two capacitors of capacitances $3\ \mu\text{F}$ and $6\ \mu\text{F}$ are charged to a potential of $12\ \text{V}$ each. They are now connected to each other with the positive plate of one joined to the negative plate of the other. The potential difference across each will be

- (1) $3\ \text{V}$ (2) Zero
(3) $6\ \text{V}$ (4) $4\ \text{V}$

72. A capacitor of $0.2\ \mu\text{F}$ capacitance is charged to $600\ \text{V}$. After removing the battery, it is connected with a $1.0\ \mu\text{F}$ capacitor in parallel, then the potential difference across each capacitor will become :

- (1) $300\ \text{V}$ (2) $600\ \text{V}$
(3) $100\ \text{V}$ (4) $120\ \text{V}$

73. Mean electric energy density between the plates of a charged capacitor is :

Here q = Charge on capacitor

A = Area of each plate of the capacitor

- (1) $q^2/(2\epsilon_0 A^2)$ (2) $q/(2\epsilon_0 A^2)$
(3) $q^2/(2\epsilon_0 A)$ (4) None of these

74. If potential difference across a capacitor is changed from $15\ \text{V}$ to $30\ \text{V}$, work done is W . The work done when potential difference is changed from $30\ \text{V}$ to $60\ \text{V}$, will be :

- (1) W (2) $4W$
(3) $3W$ (4) $2W$

75. Three capacitors each of capacity $4\ \mu\text{F}$ are to be connected in such a way that the effective capacitance is $6\ \mu\text{F}$. This can be done by :-

- (1) connecting all of them in series
(2) connecting all of them in parallel
(3) connecting two in series and one in parallel
(4) connecting two in parallel and one in series

76. A capacitor is connected to a $10\ \text{V}$ battery. The charge on plates is $40\ \mu\text{C}$ when medium between plates is air. The charge on the plates become $100\ \mu\text{C}$ when the space between the plates is filled with oil. The dielectric constant of oil is :


- (1) 2.5 (2) 4
(3) 6.25 (4) 10

77. Two capacitor each having a capacitance C and breakdown voltage V are joined in series. The effective capacitance and maximum working voltage of the combination is :-

- (1) $2C, 2V$ (2) $\frac{C}{2}, \frac{V}{2}$
(3) $2C, V$ (4) $\frac{C}{2}, 2V$

78. The charge (in μC) on any one of the $2\ \mu\text{F}$ capacitor and $1\ \mu\text{F}$ capacitor will be given respectively as :

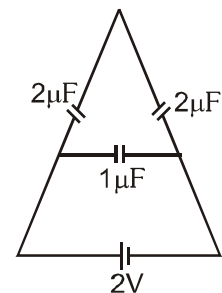- (1) $1, 2$
(2) $2, 1$
(3) $1, 1$
(4) $2, 2$



79. The electric field between the plates of a parallel plate capacitor when connected to a certain battery is E_0 . If the space between the plates of the capacitor is filled by introducing a material of dielectric constant K without disturbing the battery connections; the field between the plates will be :

- (1) KE_0 (2) E_0
(3) $\frac{E_0}{K}$ (4) None of the above

80. A $40\ \mu\text{F}$ capacitor in a defibrillator is charged to $3000\ \text{V}$. The energy stored in the capacitor is sent through the patient during a pulse of duration $2\ \text{ms}$. The power delivered to the patient is :

- (1) $45\ \text{kW}$ (2) $90\ \text{kW}$
(3) $180\ \text{kW}$ (4) $360\ \text{kW}$



- 81.** Two capacitors with capacity C_1 and C_2 , when connected in series, have a capacitance C_s and when connected in parallel have a capacitance C_p . Which of the following is true ?

(1) $C_s = C_1 + C_2$ (2) $C_p = \frac{C_1 C_2}{C_1 + C_2}$
 (3) $\frac{C_s}{C_p} = \frac{C_1}{C_2}$ (4) $C_s C_p = C_1 C_2$

- 82.** A parallel plate capacitor C has a charge q and potential V between the plates. Work required to double the distance between the plates is :

(1) $\frac{1}{2} CV^2$ (2) $\frac{1}{4} CV^2$
 (3) $\frac{1}{2} C \left(\frac{V}{2} \right)^2$ (4) CV^2

- 83.** Two metallic spheres of radii R_1 and R_2 are connected by a thin wire. If $+q_1$ and $+q_2$ are the charges on the two spheres then :

(1) $\frac{q_1}{q_2} = \frac{R_1^2}{R_2^2}$ (2) $\frac{q_1}{q_2} = \frac{R_1}{R_2}$
 (3) $\frac{q_1}{q_2} = \frac{R_1^3}{R_2^3}$ (4) $\frac{q_1}{q_2} = \frac{(R_1^2 - R_2^2)}{(R_1^2 + R_2^2)}$

- 84.** Two spheres have radii 10 cm & 20 cm. One of the sphere is given 150 μC charge and connected by a wire. Their common potential will be –

(1) 9×10^6 volts (2) 4.5×10^6 volts
 (3) 1.8×10^6 volts (4) 1.35×10^9 volts

- 85.** Total energy stored in a 900 μF capacitor at 100 volts is transferred into a 100 μF capacitor. The potential drop across the new capacitor is (in volts)

(1) 900 (2) 200
 (3) 100 (4) 300

EXERCISE-I (Conceptual Questions)										ANSWER KEY					
Que.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Ans.	1	4	3	3	1	3	4	2	4	3	4	2	4	2	1
Que.	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
Ans.	2	2	3	3	4	3	4	3	1	4	1	2	2	4	3
Que.	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
Ans.	3	3	1	4	1	3	2	2	3	1	2	3	3	1	2
Que.	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
Ans.	2	3	2	2	1	1	1	1	2	4	4	2	3	2	2
Que.	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
Ans.	1	2	2	4	4	1	1	2	3	2	4	3	1	2	3
Que.	76	77	78	79	80	81	82	83	84	85					
Ans.	1	4	4	2	2	4	1	2	2	4					



Directions for Assertion & Reason questions

These questions consist of two statements each, printed as Assertion and Reason. While answering these Questions you are required to choose any one of the following four responses.

- (A) If both Assertion & Reason are True & the Reason is a correct explanation of the Assertion.
 (B) If both Assertion & Reason are True but Reason is not a correct explanation of the Assertion.
 (C) If Assertion is True but the Reason is False.
 (D) If both Assertion & Reason are false.

1. **Assertion :-** Increasing the charge on the plates of a capacitor means increasing the capacitance.

Reason :- Because $Q = CV \Rightarrow Q \propto C$.

- (1) A (2) B (3) C (4) D

2. **Assertion :-** The capacitance of a capacitor depends on the shape, size and geometrical placing of the conductors and the medium between them.

Reason :- When a charge q passes through a battery of emf E from the negative terminal to the positive terminal, an amount of work qE is done by the battery.

- (1) A (2) B (3) C (4) D

3. **Assertion :-** A dielectric slab is inserted between the plates of an isolated charged capacitor. The charge on the capacitor will remain the same.

Reason :- Charge on an isolated system is conserved.

- (1) A (2) B (3) C (4) D

4. **Assertion :-** Two adjacent conductors carrying the same charge can be at different potentials.

Reason :- The conductors may have different sizes and hence different capacitances.

- (1) A (2) B (3) C (4) D

5. **Assertion :-** When charges are shared between two parallel plate capacitors, charge of system is conserved but some energy is lost.

Reason :- During the sharing of charges, some energy is dissipated as heat.

- (1) A (2) B (3) C (4) D

6. **Assertion:-** On filling the space between the plates of a parallel plate air capacitor with a dielectric, capacity of the capacitor is increased.

Reason :- The same amount of charge can be stored at a reduced potential.

- (1) A (2) B (3) C (4) D

7. **Assertion :-** A parallel plate capacitor is connected across a battery through a key. A dielectric slab of dielectric constant K is introduced between the plates. The energy which is stored becomes K times.

Reason :- The potential difference between the plates remains constant or unchanged.

- (1) A (2) B (3) C (4) D

8. **Assertion :-** When a capacitor is charged by a battery, both the plates receive charges equal in magnitude, no matter whether the sizes of plates are identical or not.

Reason :- The charge distribution on the plates of a capacitor is in accordance with the charge conservation principle.

- (1) A (2) B (3) C (4) D

9. **Assertion :-** If three capacitors of capacitances $C_1 < C_2 < C_3$ are connected in series and parallel, then $C_{\text{parallel}} > C_{\text{series}}$.

Reason :- $C_{\text{series}} = C_1 + C_2 + C_3$

$$\text{and } \frac{1}{C_{\text{parallel}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

- (1) A (2) B (3) C (4) D



10. Assertion :- Circuits containing high capacity capacitors, charged to high voltages should be handled with caution, even when the current in the circuit is switched off.

Reason :- When an isolated capacitor is touched by hand or any other part of the human body, there is an easy path to the ground available for the discharge of the capacitor.

(1) A (2) B (3) C (4) D

11. Assertion :- The dipoles in a dielectric are not completely aligned in weak external electric field.

[AIIMS-2016]

Reason :- Thermal energy tends to de-align them.

(1) A (2) B (3) C (4) D

12. Assertion :- Dielectric constant of metal is infinite.

[AIIMS-2016]

Reason :- Electric field inside metal is zero.

(1) A (2) B (3) C (4) D

EXERCISE-II(Assertion & Reason)

ANSWER KEY

Que.	1	2	3	4	5	6	7	8	9	10	11	12	
Ans.	4	2	1	1	1	1	1	1	3	1	1	2	

